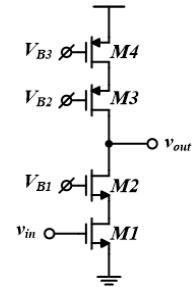



1. For the cascode amplifier below, assume all transistors have the same g_m and the same r_o . If for all transistors $V_A = 10$ V and $V_{ov} = 140$ mV, then the voltage gain in dB ($20 \cdot \log|A_v|$) is approximately equal to _____ dB.

- 1 | $A_v = G_m R_{out}$
- 2 | $G_m = g_m$ and $R_{out} = \frac{1}{2} \times g_m r_o^2$
- 3 | $A_v = \frac{1}{2} \times (g_m r_o)^2 = \frac{1}{2} \times \left(\frac{2I_D}{V_{ov}} \cdot \frac{V_A}{I_D} \right)^2 = \frac{1}{2} \times \left(\frac{2V_A}{V_{ov}} \right)^2$
- 4 | $A_v = 10204 \frac{V}{V} = 80$ dB



2. For the shown cascode amplifier, if V_{out} decrease below its minimum value, the first transistor to come out of saturation (enter triode) is _____.

- 1 | $\therefore V_{DS1}$ is defined by the strong voltage V_B
- 2 | \therefore When V_{out} decrease $\rightarrow V_{DS2}$ decrease
- 3 | \therefore M2 come out of saturation first

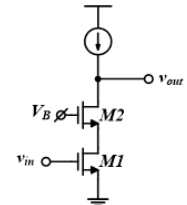


3. The cascode amplifier boosts the gain compared to a simple CS amplifier by boosting _____.

A	Rout	B	Gm	C	Rin	D	Gm and Rout
---	------	---	----	---	-----	---	-------------

4. For the shown regulated cascode amplifier, assume all transistors have the same V_{TH} and V_{ov} . The maximum output swing is achieved when V_{B2} is set to less than _____.


- 1 | maximum output swing is at $V_{out} = 2V_{ov}$
- 2 | \therefore M1 V_{DS} must be at least equal V_{ov}
- 3 | $\therefore V_{B2} = V_{GS} + V_{TH} + V_{ov}$
- 4 | $\therefore V_{B2} = 2V_{TH} + 2V_{ov}$

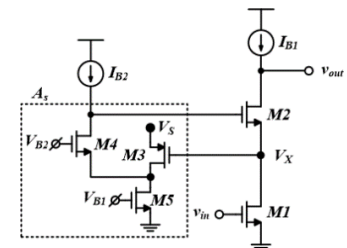

5. You are required to design an NMOS cascode that has $R_x = 500$ k ohm and $I_D = 0.5$ mA. What is the W/L that you are going to use?

Assume $\mu^*C_{ox} = 400$ $\mu A/V^2$, $V_A = 10$ V, and M1 and M2 are identical.


- 1 | $R_x = g_m r_o^2 = \frac{2I_D}{V_{ov}} \times \left(\frac{V_A}{I_D} \right)^2 = 500$ k
- 2 | $V_{ov} = 800$ mV
- 3 | $I_D = \frac{\mu^*C_{ox}}{2} \times \frac{W}{L} \times V_{ov}^2 = 0.5$ mA $\rightarrow \frac{W}{L} = 3.9$

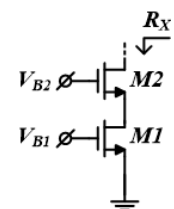

6. Assume all transistors have the same V_{ov} and same V_A , and M1 and M2 have the same bias current (hint: what is the current in M3?). R_{out} is approximately equal to $g_{m2} \cdot r_{o2}^2 / a$ where "a" is equal to _____


Hint: r_o depends on both V_A and I_D .

- 1 | M1 and M2 have same $I_D \rightarrow \therefore$ M3 has $2I_D$
- 2 | $r_{o3} = \frac{1}{2} r_{o1,2}$
- 3 | $R_{out} = r_{o1,2} \times g_{m2} \times \left(\frac{1}{2} r_{o1,2} \parallel r_{o1,2} \right) = \frac{1}{3} \times g_{m2} r_{o1,2}^2$

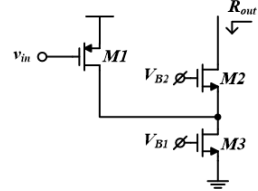


7. For the shown regulated cascode amplifier, assume all transistors have the same V_{TH} and V_{ov} . The minimum valid value for V_{B2} is equal to _____.

- 1 | $V_{B2}|_{\text{minimum}} = V_{GS4} + V_{ov5}$
- 2 | $V_{B2} = V_{TH} + V_{ov} + V_{ov}$
- 3 | $V_{B2} = V_{TH} + 2V_{ov}$

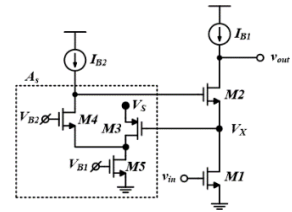


8. For the shown cascode amplifier, assume M1 and M2 have the same V_{TH} and V_{ov} . The maximum output swing is achieved when V_B is set to _____.

- 1 | maximum output swing is at $V_{out} = 2V_{ov}$
- 2 | $V_B = V_{GS} + V_{ov}$
- 3 | $V_B = V_{TH} + 2V_{ov}$

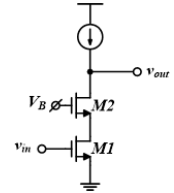

9. Assume all transistors have the same g_m and same r_o . R_{out} is approximately equal to $g_{m2} \cdot r_{o2}^2 / a$ where "a" is equal to _____

- 1 | $R_{out} = g_{m2} r_{o2} (r_{o3} \parallel r_{o1})$
- 2 | \therefore All transistors have the same g_m and $r_o \rightarrow R_{out} = \frac{1}{2} \times g_m r_o^2$
- 3 | $\therefore a = \frac{1}{2}$

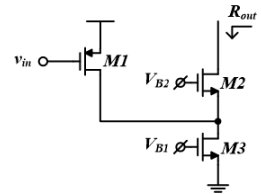

10. Assume the following:

M1 and M3 have the same bias current (hint: what is the current in M2?)

M2, M3, M4, and M5 have the same V_A (Hint: what is the relation between their r_o ?)

M3 and M4 have the same g_m (hint: do we need g_{m2} and g_{m5} to calculate the gain?)

$$g_{m1} = 2 \times g_{m3}$$

$$r_{o1} = r_{o3} / 4$$

The gain is approximately equal to $a \cdot (g_{m3} \cdot r_{o3})^2$ where "a" is equal to _____.

$$1 \mid A_v = G_m R_{out}$$

$$2 \mid \because G_m = g_{m1} = 2g_{m3}$$

$$3 \mid R_{out} = g_{m4} r_{o4} r_{o5} \parallel g_{m3} r_{o3} (r_{o2} \parallel r_{o1})$$

$$= g_{m3} r_{o3}^2 \parallel g_{m3} r_{o3} \left(\frac{1}{2} r_{o3} \parallel \frac{1}{4} r_{o3} \right) = g_{m3} \left(r_{o3}^2 \parallel \frac{1}{6} r_{o3}^2 \right) = \frac{1}{7} \times g_{m3} r_{o3}^2$$

$$4 \mid A_v = \frac{2}{7} \times (g_{m3} r_{o3})^2 = 0.29 \times (g_{m3} r_{o3})^2$$

