

① Freq Compensation


- is the modification of the system, to achieve a specific PM, to control the peaking and ringing.

- We want

$$G_x < P_x \rightarrow \omega_u < \omega_{p2}$$

We can achieve this by


I] Push ω_{p2} outwards

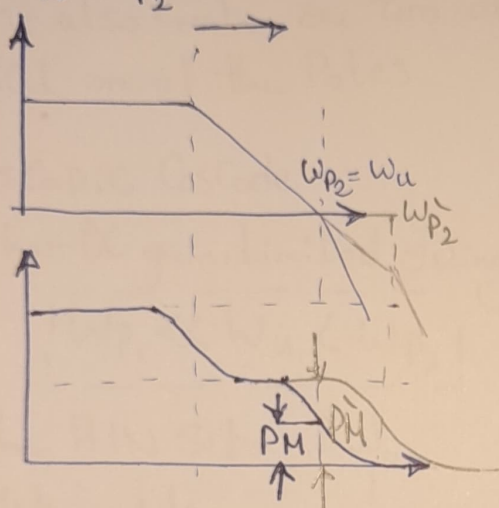

achieved by Lowering resistance or Caps @ P_2 node

→ not always feasible for free

II] Push $G_x/\omega_{p1}/\omega_u$ in

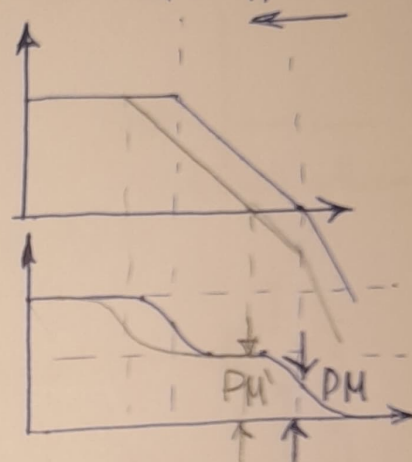

Lower GBW

∴ Lower Speed

② Single Stage OTA

I] 5T OTA

- we always want


$$[\omega_{p1} \ll \omega_u < \omega_{p2}]$$

- The HIN sets open loop BW = ω_{out}
- The First non-dominant Pole [mirror node] sets ultimate GBW, ultimate Closed loop BW [Buffer]

$$\omega_{p2} = \omega_{pM} = \frac{\omega_{m3}}{C_M} = \omega_T/3$$

$$\omega_T = 1/(C_{db1} + C_{db2} + f(C_{gdH}) + C_{gs4} + C_{gs3} + C_{db1})$$

higher Caps

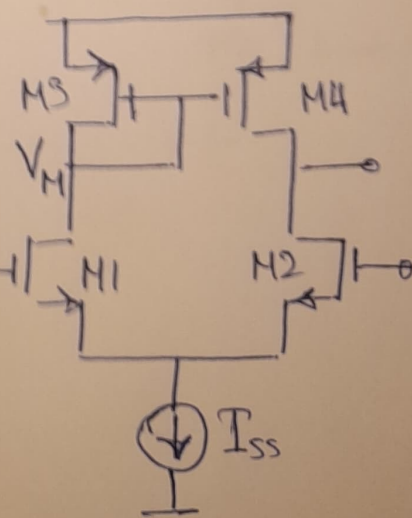


- The LHP zero

$\omega_z = 2\omega_{p2} \rightarrow$ reduce the effect of P_2

- if Fully diff.?

* out^+ and out^- Contribute 1 Pole

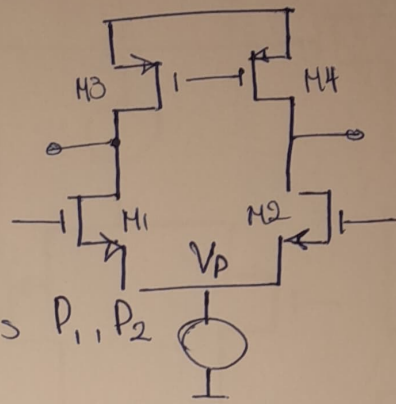
* $(\omega_{p2}) = \frac{g_m}{C_L}$
at V_P



* if there is a mismatch

- out^+ and out^- Contribute two Poles P_1, P_2 which are close to each other

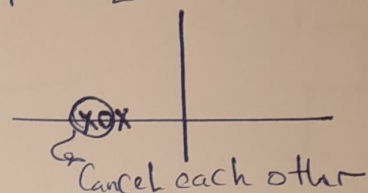- it also create one zero at $\omega_z = 2[\omega_{p1}, \omega_{p2}]$
Cancel one of the Poles



12] Telescopic Cascode

- Higher DC gain, Limited swing, additional Poles

- $|\omega_{p1}| \ll \omega_u < \omega_{p2}$

- the HIN sets BW_{OL}

$$\omega_{p1} = \omega_{pout} = \frac{1}{R_{out} C_{out}}$$

- V_x and V_y Contribute a single Pole


non-dominant Pole Considerations.

PMOS Contribute Larger

Caps \rightarrow For same I_D , $\omega_{PMOS} \uparrow$, $C_{PMOS} \uparrow$


$\approx C_{gs}$ is Larger than other Caps
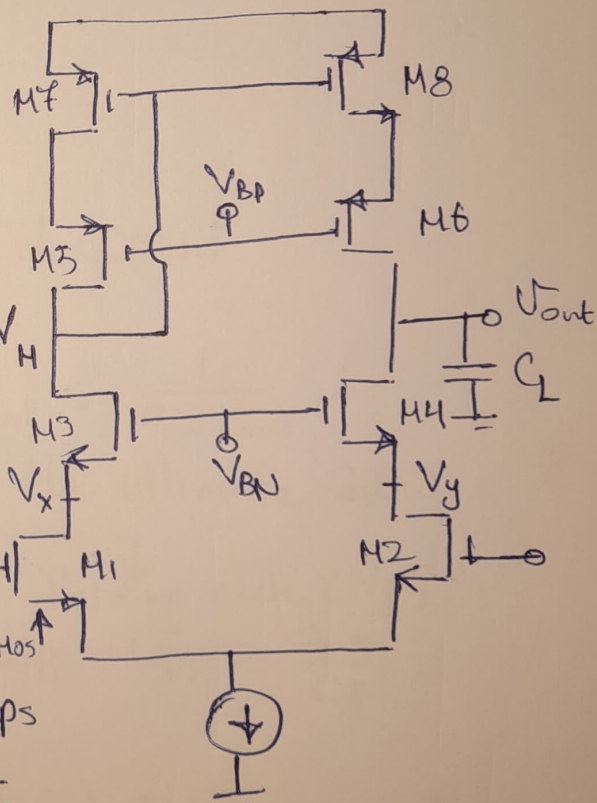
$$\omega_{p2} = \omega_{pH} = \frac{g_{m7}}{C_H} = \frac{\omega_T}{4}$$



[3] Folded CasCode

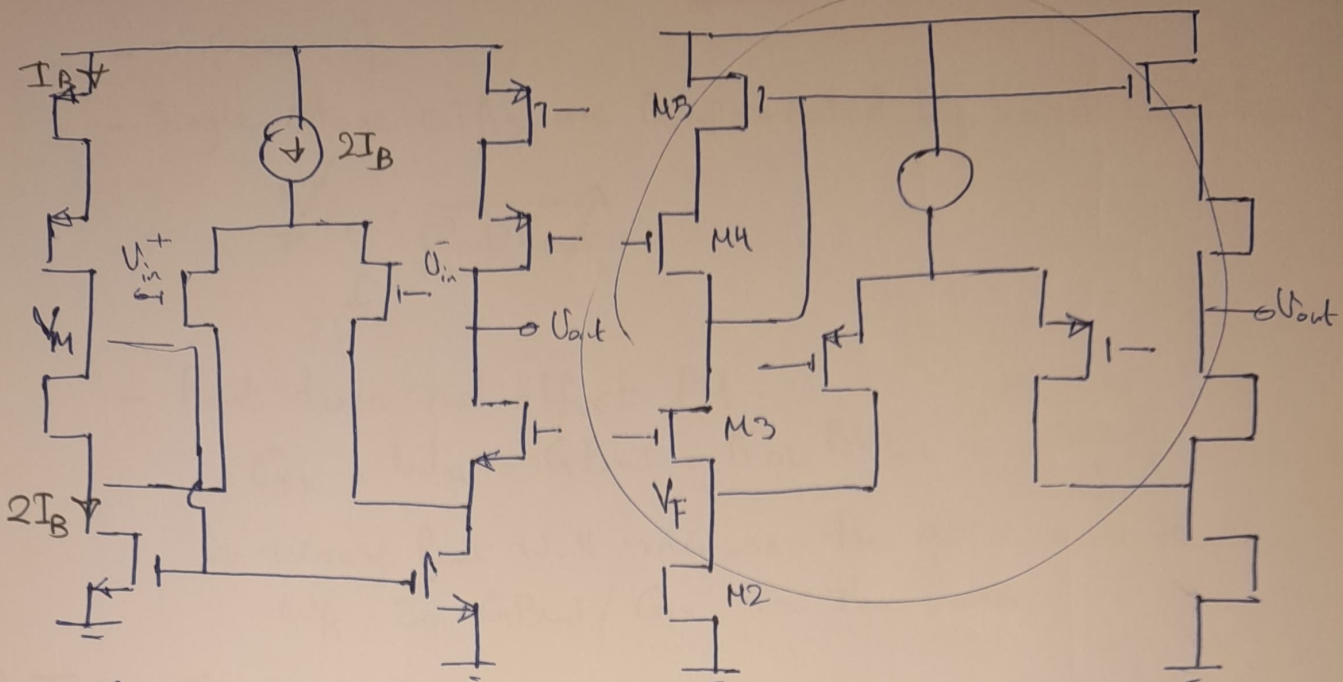- Two Possible implementation for SE output



- Compared to Telescopic CasCode

* More Power $2\times$

* Lower gain $[r_{o1} || r_{o2}]$

* More node / Poles

* More Complex

** input and output range decoupled

- $\omega_{P1} \ll \omega_u < \omega_{P2}$

- the HIN sets BW_{OL} , $\omega_{P1} = \omega_{Pout} = \frac{1}{R_{out} C_{out}}$

- the first non-dominant Pole sets the ultimate GBW

mirror node (V_M)
 $\omega_{P2} = \omega_{PM} = \frac{g_{m3}}{C_M}$

folding node (V_F)
 $\omega_{P2} = \omega_{PF} = \frac{g_{m3}}{C_F}$

- Consideration

- M2 has Large Capacitance (double the current)

* Single-Stage OTAs: Compensation.

- Push G_x / W_u / W_{p1} \rightarrow inwards : Lower GBW \leftarrow
- increase Q
- Single stage OTAs are Compensated by Load Capacitance

$$\cancel{W_{p1}} = \frac{1}{(R_{out} C_{out})}$$

??

- R_{out} does not affect PM

$$G_x = W_u = GBW = A_{OL} BW_{OL} = \frac{G_m}{C_{out}}$$

\rightarrow increase R_{out} will increase the gain and reduce W_{p1} , so GBW / G_x is the same

③ Two-Stage OTA

- isolates the gain and swing requirements.
 - * But much more Power Consumption
 - * And Complicates stability requirements
- Three stage OTA exists, but quite difficult to stabilize
- First stage can be 5T-OTA [Moderate gain] or Cascode [high gain]
- Second stage is typically a simple Common-Source
 - \rightarrow allows maximum swing


\rightarrow Two gain stages \rightarrow two HIN
 \rightarrow two dominant Poles


1 internal Pole, $W_{p1} = \frac{1}{R_{out1} C_1}$

2 output pole, $W_{p2} = \frac{1}{R_{out2} C_2}$

Solutions

use miller

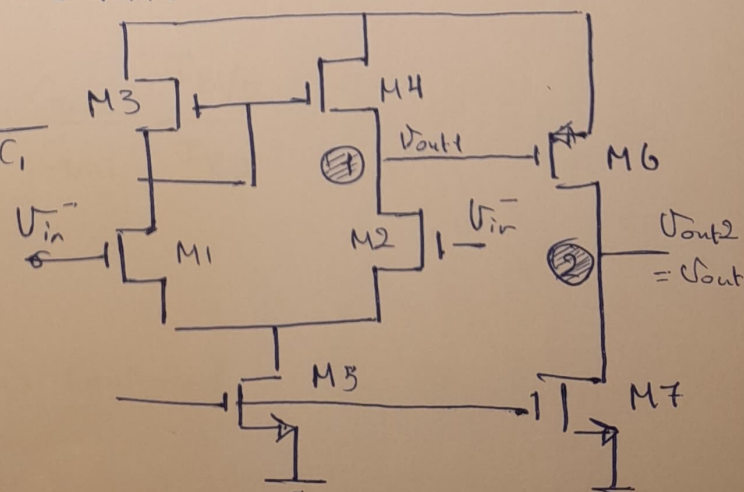

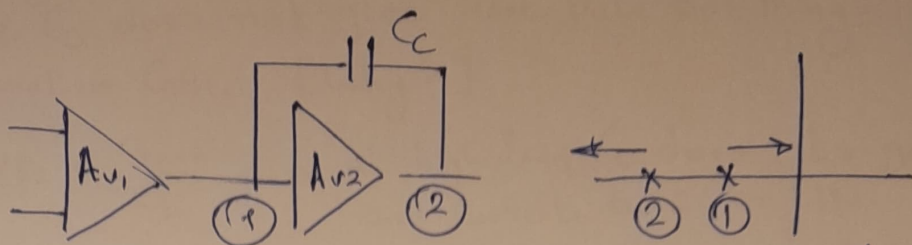

- C_c has miller effect at node ① $\rightarrow C_{c1} \uparrow, \omega_{p1} \downarrow$

\hookrightarrow Push G_{ix} inwards $\neq \omega_{p1} = \frac{1}{R_{out1} [G_{m2} R_{out2}] C_c}$

- Push ω_{p2} outwards [how?]

a) high freq C_c is short circuit

\therefore Node ② become LIN $\sim \frac{1}{g_m}$

$$\therefore \omega_{pnd} \approx \omega_{p2} = \frac{G_{m2} C_c}{C_c [C_1 + C_2] + C_1 C_2} \approx \frac{G_{m2}}{C_1 + C_2} = \frac{G_{m2}}{C_L}$$

$$\begin{aligned} - \text{GBW} &\approx G_{m1} R_{out1} G_{m2} R_{out2} \cdot \frac{1}{R_{out1} [G_{m2} R_{out2}] C_c} \\ &= \frac{G_{m1}}{C_c} \end{aligned}$$

- For Critical damped response, $\zeta = 1, Q = 0.5$
PM = 76°

$$\therefore \omega_{p2} \approx 4 \omega_{u1} \rightarrow \frac{G_{m2}}{C_L} \approx \frac{4 G_{m1}}{C_c}$$

- Assume $C_c = C_L / 2$

$$\therefore \frac{G_{m2}}{C_L} \approx \frac{8 G_{m1}}{C_L} \rightarrow \frac{G_{m2}}{G_{m1}} = 8$$

- For same g_m / I_D

$$\therefore \frac{G_{m2} / I_{B2}}{G_{m1} / \frac{I_{B1}}{2}} = \frac{G_{m2}}{G_{m1}} \frac{I_{B1}/2}{I_{B2}} = 1 \rightarrow \frac{I_{B1}}{I_{B2}} = \frac{1}{4}$$

$$\therefore I_{B2} = 4 I_{B1}$$

- 80% of the Power is Consumed in the second stage to achieve stability

\therefore 80% of the Current not contribute to GBW

\therefore miller OTA is very energy inefficient

- Too Large C_c does not give more Pole Splitting
: Just Smaller GBW [Why?]

$\rightarrow \omega_{p2} \approx \frac{G_{m2}}{C_L} \rightarrow$ at high freq C_c does its job and converts out2 to LIN


- Reasonable Starting Point $C_c \approx 0.8 : 0.5 C_L$

- 'increasing' G_{m2} works even better than increasing C_c

$$\omega_{p1} = \frac{1}{R_{out1} [G_{m1} R_{out2}] C_c}, \quad \omega_{p2} \approx \frac{G_{m2}}{C_1 + C_2} \approx \frac{G_{m2}}{C_L}$$

\rightarrow But more Power Consumption in the second stage

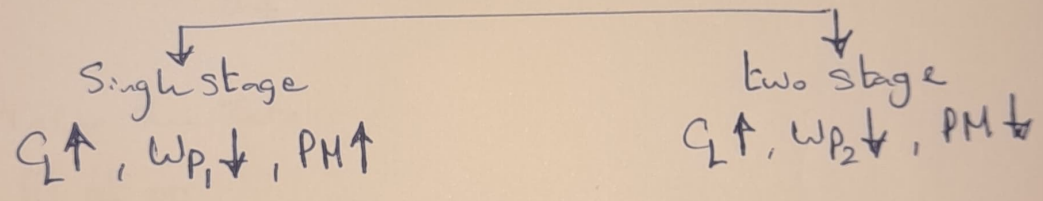- Single ~~ended~~ stage Vs Two stage Sensitivity to C_L



4) The feedforward zero \rightarrow Reminder

$V_{out} = 0, I_{out} = 0$


$\Rightarrow V_{in} s C_F = -G_m V_{in}$

$\Rightarrow s_Z = -\frac{G_m}{C_F}$

\rightarrow LHP zero if G_m is +ve ✓

\rightarrow RHP zero if G_m is -ve ✗

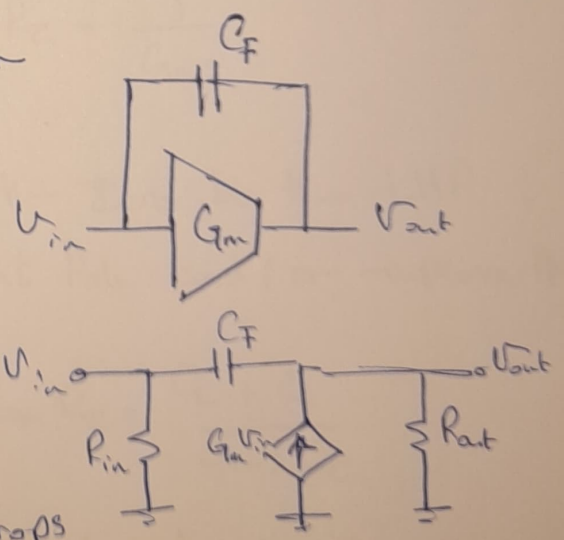\rightarrow mag increase and Phase drops
 \rightarrow very bad for FB Loop stability



- RHP zero is bad for both magnitude and phase
 - ↳ Pushes G_m outwards and Pushes P_m inwards
 - ↳ Increasing C_c may hurt stability


$$\omega_z = \frac{g_{m6}}{C_c + C_d} \approx \frac{g_{m2}}{C_c}$$

- Handling the RHP zero

↳ Add a resistance to control the value of the zero

$$\frac{V_{out1}}{R_z + \frac{1}{s_z C_c}} = g_{m6} V_{out}$$
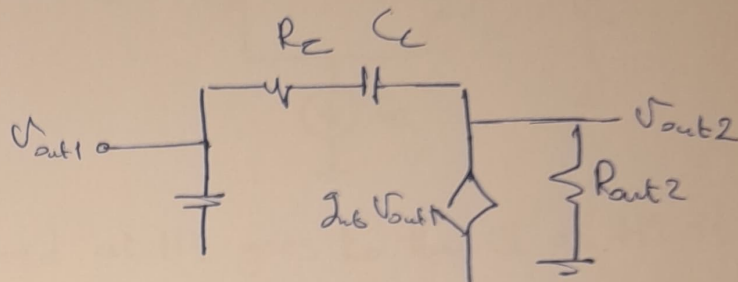
$$s_z = \frac{1}{C_c \left[\frac{1}{g_{m6}} - R_z \right]}$$



- Place the zero

[1] at ∞

$$\omega_z = \frac{1}{C_c \left[\frac{1}{g_{m2}} - R_z \right]} \rightarrow R_z = \frac{1}{g_{m2}}$$

[2] Some designers try to move the zero to the LHP to cancel the first non-dominant pole and/or improve AM

$$\frac{1}{C_c \left(R_z - \frac{1}{g_{m2}} \right)} = \frac{g_{m2}}{C_L} \rightarrow R_z = \frac{C_L + C_c}{g_{m2} C_c}$$

* Practically never achieved due to variation

* actually does not lead to faster response (Why?)

Critical damped [second order system]

faster than over damped [1st order system]

* Pole-zero doublet: Pushing the LHP zero to lower freq



↳ Very poor settling time
↳ noise amplification

⑤ Slew Rate (SR)

- is the maximum rate at which the output of an opamp changes when a large differential input signal is present

III Single stage Slew Rate

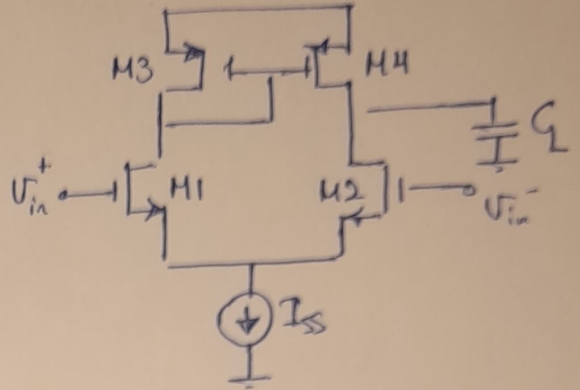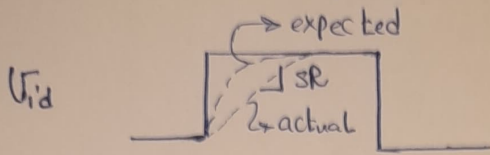- if $V_{in}^+ \uparrow, V_{in}^- \downarrow$



$$I_D \propto M1 \uparrow, I_D \propto M2 \downarrow$$

\rightarrow M1: Comply ON

M2: Comply off

$\therefore I_{D1} = I_{SS}$ will be mirrored at M4 goes to the CL as M2 is off
off $SR = I_{SS} / C_L$

and vice versa if $V_{in}^+ \downarrow, V_{in}^- \uparrow$

II Two stage OTA Slew Rate

~~FX~~ miller Compensated

if V_{id} is large

$$\therefore SR = \frac{I_{clmax}}{C} = \frac{I_{SS}}{C}$$

$$\therefore \omega_u = \frac{g_m}{C}, I_{SS} = 2I_{D1}$$

$$\therefore SR = \frac{2I_{D1} \omega_u}{g_{m1}} \rightarrow \text{II}$$

$$\therefore g_{m1} \approx \sqrt{\mu C_{ox} \frac{W}{L} \cdot 2I_{D1}}$$

$$\therefore V_{ov} = \sqrt{\frac{2I_{D1}}{\mu C_{ox} \frac{W}{L}}}$$

$$\therefore SR = \frac{2I_{D1}}{\sqrt{\mu C_{ox} \frac{W}{L} \cdot 2I_{D1}}} \omega_u = \frac{V_{eff}}{2V_{ov}} \omega_u$$

$$\therefore \frac{2}{V^*} = \frac{g_m}{I_D} \rightarrow \frac{2I_D}{g_m} = V^* \rightarrow SR = V^* \omega_u$$

