

Spec.			
5T - OTA			
Supply Voltage	1.2 V	Power Consumption	$\leq 30 \text{ uW}$
Open loop DC voltage gain	$\geq 36 \text{ dB}$	Reference current	10 uA
CMRR @ DC	$\geq 50 \text{ dB}$	Linear Range	90 mVpp
BW	$\geq 100 \text{ kHz}$	Load	2 pF

- Steps





- Design of input transistors

01 | $P_{\text{cons}} = V_{DD} I_{SS} \leq 30 \text{ uW} \rightarrow I_{SS} \leq 25 \text{ uA}$

02 | $GBW = \frac{g_{m1}}{2\pi C_L} \geq 6.4 \text{ MHz} \rightarrow g_{m1} \geq 80.5 \text{ uS} \rightarrow \left(\frac{g_m}{I_D}\right)_1 \geq 6.44 \rightarrow \left(\frac{g_m}{I_D}\right)_1 = 19 \rightarrow g_m = 237.5 \text{ uS}$



03 | $A_v = g_m R_{\text{out}} = 64 \rightarrow R_{\text{out}} = r_{o1} || r_{o2} = \frac{r_o}{2} \rightarrow r_o = 539 \text{ k}\Omega \rightarrow \left(\frac{g_m}{g_{ds}}\right)_1 \geq 128$

04 | $L_1 = 3 \text{ um}, V_{GS1} = 314.5 \text{ mV}, W_1 = 43.74 \text{ um}, V_{\text{dsat}1} = 68.91 \text{ mV}$

    

- Diode connected load



05 | $r_{o2} = 539 \text{ k}\Omega$, assume $g_{m1} = g_{m2} = 237.5 \text{ uS} \rightarrow \left(\frac{g_m}{g_{ds}}\right)_2 = 19 \rightarrow L_2 = 1.68 \text{ um}, W_2 = 84.95 \text{ um}$

  

- Current mirror



06 | $A_{VCM} = \frac{1}{2g_m R_{ss}} = (50 - 36) \text{ dB} = 0.1995 \rightarrow R_{ss} = 10.6 \text{ k}\Omega$

07 | Assume M_3 biased in SI (gmoverid = 10) $\rightarrow L_3 = 180 \text{ nm}, W_3 = 760.5 \text{ nm}$

  


Simulation Results

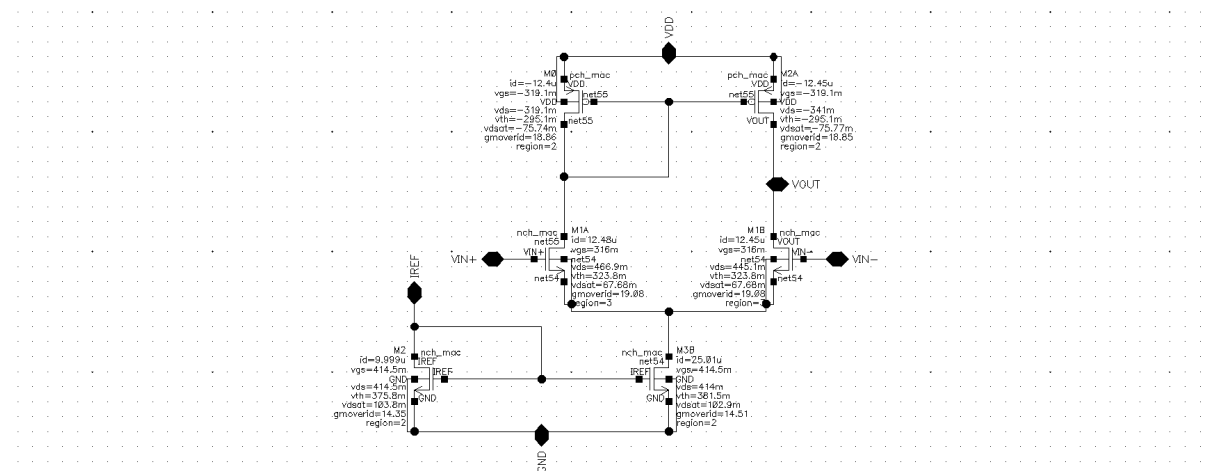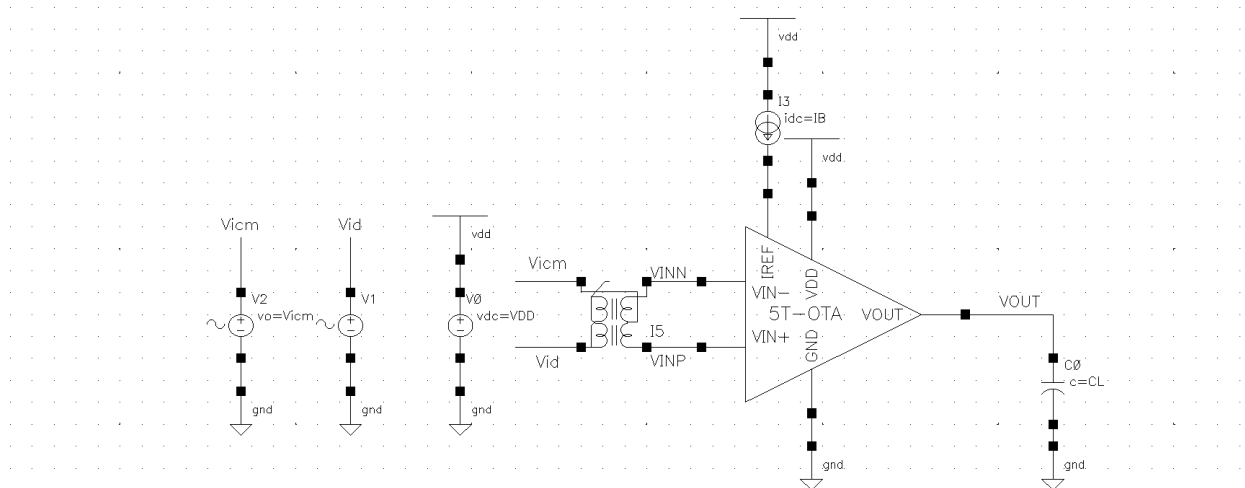
1. DC operating points and Circuit Test Bench




2. Diff Small Signal Analysis

 

3. CM Small Signal Analysis

 

4. Diff Large Signal

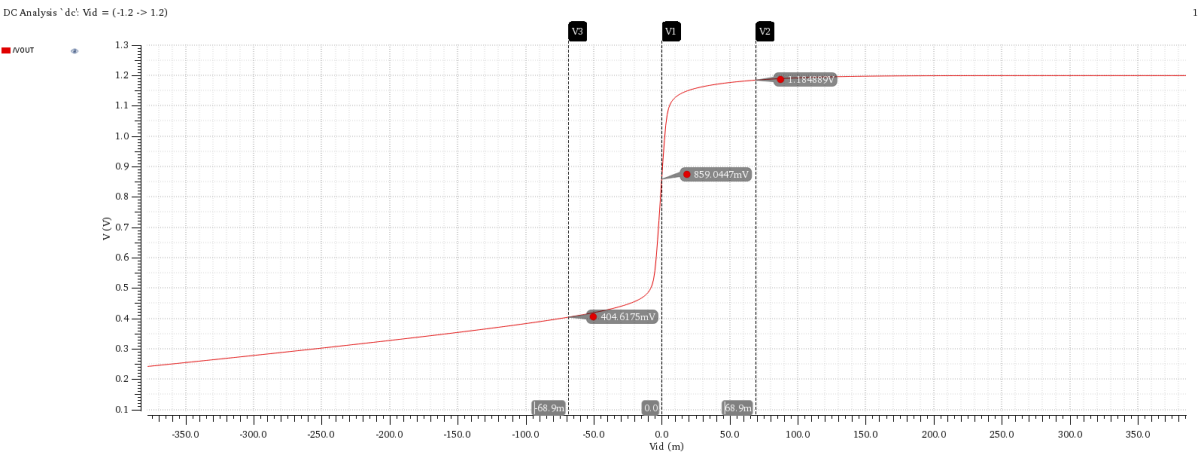

5. CM Large Signal

