

① For the shown amplifier.

If $C_L \gg C_p$ and it's required to double BW without changing the gain, the designer should

$$\therefore A_v = g_m (r_{o2} \parallel r_{o4}), BW = \frac{1}{2\pi C_L (r_{o2} \parallel r_{o4})}$$

\therefore to double the BW $\rightarrow r_o$ must be halved

$$\therefore r_o = \frac{V_A}{I_D} \rightarrow I_D \text{ doubled} \rightarrow I_{SS} \text{ doubled}$$

but $A_v \propto r_o$

$\therefore g_m$ must be doubled to keep A_v fixed

$$g_m = \sqrt{2\mu_n C_{ox} \frac{W}{L} \cdot 2I_D}$$

$$\text{If } I_D \times 2 \rightarrow g_m \times \sqrt{2}$$

$$\therefore \text{We should double the } W \rightarrow g_m \times \sqrt{2} \times \sqrt{2} \rightarrow g_m \times 2$$

\therefore double I_{SS} and double $W_{1,2}$

② If I_{SS} is decreased and W is changed such that V_{ov} is kept fixed, then the gain...



$$\therefore A_v = g_m \frac{r_o}{2} \text{ (assume } r_{o2} = r_{o4} \text{ for simplicity)}$$

$$\therefore A_v = \frac{2I_D}{V_{ov}} \times \frac{V_A}{I_D} \times \frac{1}{2} = \frac{V_A}{I_D} \cdot \frac{I_D}{V_{ov}} = \frac{V_A}{V_{ov}} \neq f(I_D) \dots$$

$\therefore V_A, V_{ov}$ is fixed $\rightarrow A_v$ remains unchanged.

③ $V_{DD} = 2$, $V_{TH} = 0.4$ and $V_{ov} = 0.2$, then $V_{out} = ?$
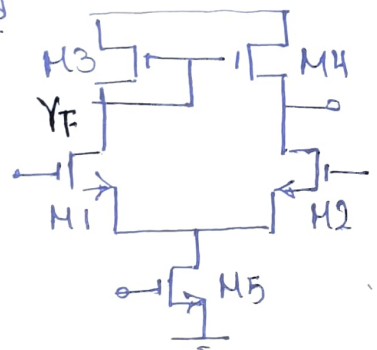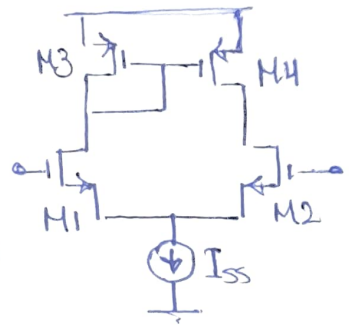
$$V_{out} = V_F = V_{DD} - V_{SG3,4} = 1.4 \text{ V}$$



- (4) it's required to improve the low freq CMRR without affecting the DC gain or the tail current source, the designer should

$$\infty \text{ CMRR} = \frac{g_{m1,2} (r_{o2} \parallel r_{o4})}{2 \text{ DC gain}} \times \frac{2 g_{m3,4} R_{SS}}{2 \text{ tail current source}}$$

\therefore We need to improve $g_{m3,4}$

$$\infty g_m = \sqrt{\mu C_{ox} \frac{W}{L} 2 I_D} \rightarrow \text{We can improve by } \begin{cases} \rightarrow \text{Increase } W \\ \rightarrow \text{reduce } L \text{ (not valid)} \end{cases}$$

as it affect tail current source.

- (5) Assume symmetry and all transistors have same V_A

The gain of the shown amp is


$$\infty i_x = i_4 + i_2 = \frac{V_x}{r_{o4}} + \frac{V_x}{2r_{o1,2}} = V_x \left(\frac{1}{r_o} + \frac{1}{2r_o} \right)$$

$$\infty R_{out} = \frac{V_x}{i_x} = \frac{2}{3} r_o$$

$$\infty G_m = \frac{i_{outsc}}{V_{GS}} \rightarrow i_{outsc} = g_{m2} V_{GS2} = g_{m2} \frac{V_{in}}{2}$$

$$\infty G_m = \frac{g_{m2}}{2}$$

$$\infty A_v = \frac{g_{m2} r_o}{3}$$

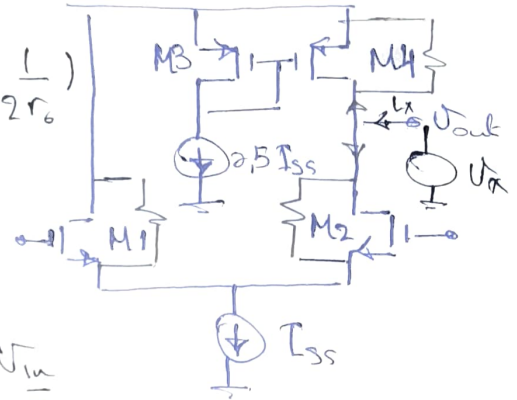

- (6) $V_{DD} = 2$, $V_{TH} = 0.4$, $V_{ov} = 0.2$, $V_{id} = 5\text{mV}$ then $V_{out} = ?$

$$\infty V_{out} = V_{outCM} + V_{out} = V_{DD} - V_{SG3,4} + A_v V_{id}$$

$$\infty A_v = g_m \frac{r_o}{2} = \frac{V_A}{V_{ov}} = 50$$

$$\infty V_{out} = 1.4 + 25\text{mV} = 1.65\text{V}$$

- (7) $V_{DD} = 2$, $V_{ov} = 0.2 \rightarrow$ max peak to peak output swing is --

$$\infty 2V_{ov} \leq V_{out} \leq V_{DD} - V_{ov}$$

$$\infty 0.4 \leq V_{out} \leq 1.8 \rightarrow \text{max swing} = 1.8 - 0.4 = 1.4\text{V}$$


⑧ If I_{SS} is decreased and the sizing is kept fixed then the gain --

$$A_v = G_m R_{out} = g_m \frac{r_o}{2} = \frac{V_A}{V_{OV}}$$

If $I_{SS} \downarrow$, $V_{OV} \downarrow$

$$\text{Where } I_D = \mu C_{ox} \frac{W}{L} V_{OV}^2$$

$\therefore A_v$ will increase

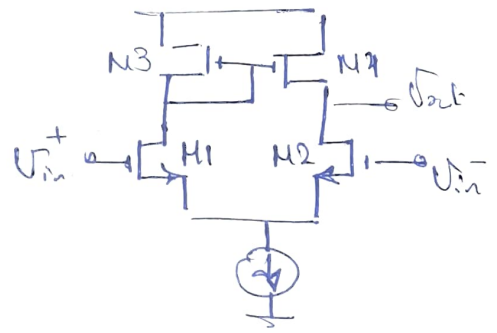

⑨ If $V_{DD} = 2V$, $V_{TH} = 0.4V$ and $V_{OV} = 0.2V$, the max CM input voltage is -- V

$$\begin{aligned} V_{ICM \max} &= V_{GS1,2} - V_{OV1,2} - V_{GS3,4} + V_{DD} \\ &= \cancel{V_{TH}} + \cancel{V_{OV}} - \cancel{V_{OV}} - \cancel{V_{TH}} - V_{OV} + V_{DD} \\ &= 2 - 0.2 = 1.8V \end{aligned}$$

⑩ If $V_{DD} = 2V$, $V_{TH} = 0.4$, $V_{OV} = 0.2$; $V_A = 10V$ and $V_{in1} = 1V$, if V_{out1} is connected to V_{in2} , then the voltage at V_{out} is --

$$\therefore V_F = V_{DD} - V_{SG3,4} = 2 - 0.4 - 0.2$$

$$V_F = 1.4$$

$$\therefore V_{out} = V_{in2}$$

$$\therefore V_{offset} = 1.4 - 1 = 0.4V$$

$$\therefore A_v = g_m \frac{r_o}{2} = \frac{V_A}{V_{OV}} = 50$$

$$\therefore \text{input referred offset} = \frac{0.4}{50} = 8mV$$

$$\therefore V_{out} = 1 + 8mV = 1.008V$$

