

3. Basic Amplifier Stages


1. The multistage amplifier that gives high input impedance and low output impedance is the ____.

A	CS and CD	B	All are wrong	C	CG and CD	D	CS and CG
---	-----------	---	---------------	---	-----------	---	-----------

$$A_v = G_m R_{out} = g_m \times R_D$$

The device need at least $V_{DS} = V_{ov}$ to work in saturation
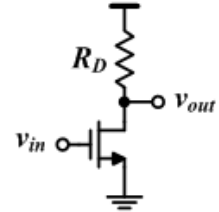
$$A_v = \frac{2I_D}{V_{ov}} \times \frac{V_{DD} - V_{ov}}{I_D} = 2 \left(\frac{V_{DD}}{V_{ov}} - 1 \right)$$



2. The maximum absolute

voltage gain of the shown CS amplifier can be written as ____.

A	$(V_{DD}/V_{ov} - 1)$	B	$2 \cdot (V_{DD}/V_{ov} - 2)$	C	$(V_{DD}/V_{ov} - 2)$	D	$2 \cdot (V_{DD}/V_{ov} - 1)$
---	-----------------------	---	-------------------------------	---	-----------------------	---	-------------------------------


3. Assume $L_1 = 2 \cdot L_2$. Neglect body effect and V_A dependence on terminal voltages. R_X is

$$R_X = r_{o2}(1 + g_{m2}R_{LFD1})$$

$$R_{LFD1} = r_{o1}$$

if $L_1 = 2 \cdot L_2 \rightarrow r_{o1} = 2 \cdot r_{o2}$
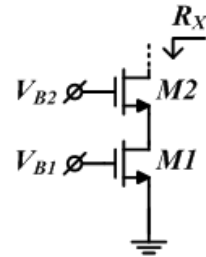
$$R_X = r_{o2} \times g_{m2} \times 2r_{o2} = 2 g_{m2}r_{o2}^2$$



approximately given by ____.

A	$2 \cdot g_{m2} \cdot r_{o2}^2$	B	$4 \cdot g_{m2} \cdot r_{o2}^2$	C	$g_{m2} \cdot r_{o2}^2$	D	$0.5 \cdot g_{m2} \cdot r_{o2}^2$
---	---------------------------------	---	---------------------------------	---	-------------------------	---	-----------------------------------

4. The basic MOS amplifier stage that provides power gain is the ____.

A	CS	B	CG	C	CD	D	All
---	----	---	----	---	----	---	-----

5. If a voltage signal has 10mV amplitude superimposed on 0.3V dc level, and it is required to shift the dc level to be 0.9V without changing the signal amplitude, then ____ amplifier should be used.

A	NMOS CS	B	PMOS CD	C	NMOS CD	D	PMOS CS
---	---------	---	---------	---	---------	---	---------

6. The basic MOS amplifier stage that practically always has absolute voltage gain < 1 is the ____.

A	CS	B	CG	C	CD	D	All are wrong
---	----	---	----	---	----	---	---------------

7. The multistage amplifier that gives high input impedance and high voltage gain is ____.

A	CS + CG	B	CG + CD	C	CG + CS	D	All are wrong
---	---------	---	---------	---	---------	---	---------------

8. Assume $V_{ov1} = 2 \cdot V_{ov2}$ and $L_1 = 2 \cdot L_2$. Neglect body effect and V_A dependence on terminal voltages. R_X is approximately given by ____.


$$R_X = \frac{1}{g_{m1}} \left(1 + \frac{R_{LFD2}}{r_{o1}} \right) \text{ and } R_{LFD2} = r_{o2}$$

$$\text{if } L_2 = 2 \cdot L_1 \rightarrow r_{o2} = 2 \cdot r_{o1}$$

$$R_X = \frac{1}{g_{m1}} \left(1 + \frac{r_{o2}}{r_{o1}} \right) = \frac{3}{g_{m1}}$$

A	$2 \cdot g_{m1} \cdot r_{o1}^2$	B	$4 \cdot g_{m1} \cdot r_{o1}^2$	C	$g_{m1} \cdot r_{o1}^2$	D	$0.5 \cdot g_{m1} \cdot r_{o1}^2$
---	---------------------------------	---	---------------------------------	---	-------------------------	---	-----------------------------------

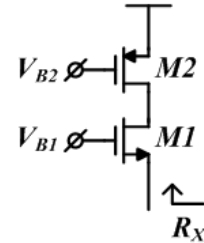9. Assume $g_m \cdot r_o \gg 1$ and $L_2 = 2L_1$. Neglect body effect and assume V_A does not depend on terminal voltages. R_X is given by ____.



A	$2/g_{m1}$	B	$4/g_{m1}$	C	$1/g_{m1}$	D	$3/g_{m1}$
---	------------	---	------------	---	------------	---	------------

10. The basic MOS amplifier stage that practically always has absolute current gain < 1 is the ____.

A	CS	B	CG	C	CD	D	All are wrong
---	----	---	----	---	----	---	---------------

$$R_X = r_{o2}(1 + g_{m2}R_{LFD1}) \text{ and } R_{LFD1} = r_{o1}$$

$$\text{if } L_1 = 2 \cdot L_2 \rightarrow r_{o1} = 2 \cdot r_{o2} \text{ and if } V_{ov1} = 2 \cdot V_{ov2} \rightarrow g_{m1} = \frac{1}{2}g_{m2}$$

$$R_X = \frac{r_{o1}}{2} \times 2g_{m1} \times r_{o1} = g_{m1}r_{o1}^2$$

