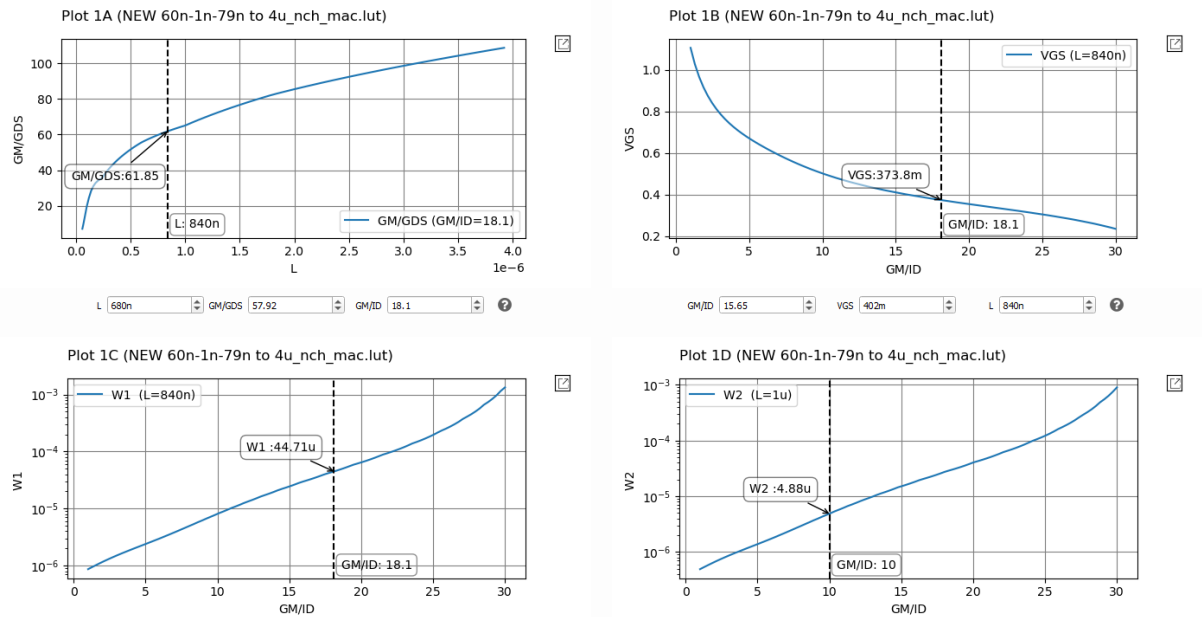


Spec.	
Common Gate (CG) Amplifier	
DC Gain	20 dB
BW	$\geq 14$ MHz
Power Consumption	$\leq 70$ uW
Cap Load	1 pF


- Steps

- 1 |  $P_{\text{cons}} = V_{DD} I_D \leq 70 \text{ uW} \rightarrow I_D \leq 58 \text{ uA}$
- 2 |  $GBW = \frac{g_m}{2\pi C_{\text{out}}} \geq 10 * 14 \text{ MHz} \rightarrow g_m \geq 880 \text{ uS} \rightarrow g_m = 1.05 \text{ mS} \rightarrow \frac{g_m}{I_D} = 18.1$
- 3 |  $A_v = g_m R_{\text{out}} = 10 \rightarrow R_{\text{out}} = 9.6 \text{ k}\Omega \rightarrow R_D = 11.5 \text{ k}\Omega \rightarrow r_o \geq 58.1 \text{ k}\Omega \rightarrow \frac{g_m}{g_{ds}} \geq 61$
- 4 |  $V_{\text{out}} = V_{DD} - I_D * R_D = 1.2 - 58\text{u} * 11.5\text{k} = 0.533 \text{ V}$
- 5 | Assume  $V_{\text{out}}$  divided equally between M1 and M2
- 6 |  $L_1 = 840 \text{ nm}, V_{GS1} = 373.8 \text{ mV}, W_1 = 44.71 \text{ um}$
- 7 | For the Current source assume long L and bias it in SI to achieve large output resistance
- 8 |  $L_2 = 1 \text{ um}, W_2 = 4.88 \text{ um}$



## - Results

### 1. DC Operating Points

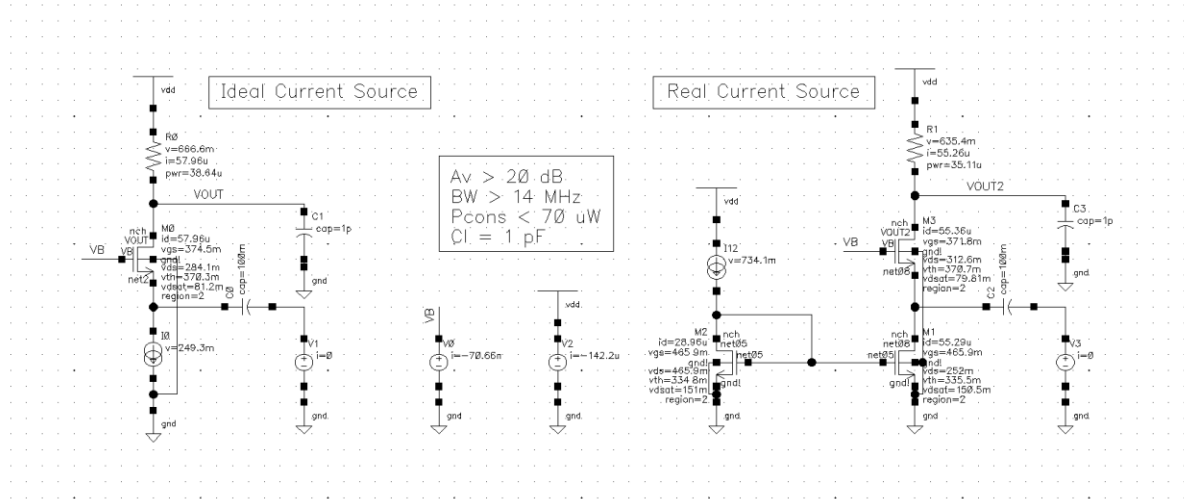

### 2. AC Analysis

AC Analysis 'ac' freq = (1 Hz -> 10 GHz)

