

5T OTA Design Example

1. If V_A slightly decreases with g_m/I_D , the chart of $g_m \cdot r_o$ vs g_m/I_D will be ____.

A	Curves with slightly decreasing slopes convex upwards	C	All answers are wrong
B	Straight lines	D	Curves with slightly increasing slopes convex downwards

2. If the long channel model (square-law) is valid, then V_{GS} vs g_m/I_D chart should be ____.

A	All answers are wrong	C	Multiple curves with shortest L at top
B	Multiple curves with longest L at top	D	A single curve independent of L

$$I_D = \frac{\mu C_{ox}}{2} \times \frac{W}{L} V_{ov}^2 \rightarrow g_m = \mu C_{ox} \times \frac{W}{L} V_{ov} \rightarrow \frac{g_m}{I_D} = \frac{2}{V_{ov}} = \frac{2}{V_{GS} - V_{TH}} \neq f(L) \rightarrow \text{single curve}$$


3. If $V_{DD} = 2V$ and the required CMIR of an OTA is 0.2 V to 1.8 V, then the input stage should be ____.

A	NMOS and PMOS (both of them together)	C	PMOS
B	NMOS	D	NMOS and PMOS (anyone of them will work)

4. For a 5T OTA, if you want to use larger g_m/I_D for the current mirror load while keeping the amplifier DC gain almost unchanged, this means you should use ____.

Hint: Neglect V_A variation with g_m/I_D .

A	Smaller W	B	Larger W	C	Larger L	D	Smaller L
---	-----------	---	----------	---	----------	---	-----------

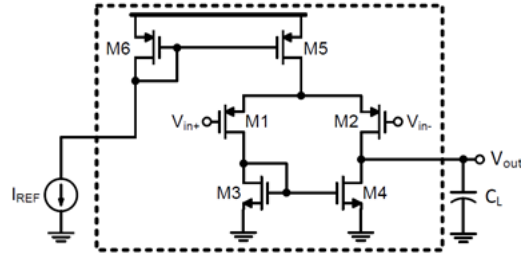

5. For the shown 5T OTA, increasing L will increase the DC voltage gain and improve the matching at the expense of ____.

A	Lower phase margin	B	Larger area	C	All are correct	D	Larger device caps
---	--------------------	---	-------------	---	-----------------	---	--------------------

Increasing $L \rightarrow$ Increase Area \rightarrow Increase device capacitances \rightarrow Increase $C_{mirr} \rightarrow$ Reduce the PM

6. For the shown 5T OTA, the g_m/I_D of ____ is a design parameter that affects the output swing.

A	$M_{3,4}$	B	All are correct	C	M_5	D	$M_{1,2}$
---	-----------	---	-----------------	---	-------	---	-----------

7. For the shown 5T OTA, if C_L is much larger than device capacitors, the main design parameter affecting the relation between power consumption and the GBW is ____.

A	L of the input pair	B	g_m/I_D of the input pair	C	L of the load	D	g_m/I_D of the load
---	---------------------	---	-----------------------------	---	---------------	---	-----------------------

$$GBW = \frac{g_{m1,2}}{2\pi C_L} \rightarrow \text{for a given } I_D \text{ the GBW achieved depends on the } g_m \text{ chosen for the input pair}$$

8. For the shown 5T OTA, using ____ will cause more CMRR degradation at high frequency.

A	Larger L for $M_{1,2}$	B	All answers are correct	C	Larger g_m/I_D for $M_{1,2}$	D	Larger g_m/I_D for M_5
---	------------------------	---	-------------------------	---	--------------------------------	---	----------------------------

$$CMRR = g_{m1,2} [r_{o2} \parallel r_{o4}] \times 2g_{m3,4} R_{ss}$$

$C_{sb1,2}$ will increase as $M_{1,2}$ area increase by larger L or larger $\frac{g_m}{I_D}$ (W) reducing

Larger $\frac{g_m}{I_D}$ (W) for $M_5 \rightarrow$ larger area for $M_5 \rightarrow$ larger C_{gd5} and C_{db5}

All these capacitance are parallel with R_{ss} reducing the effective R_{ss}

9. For the shown 5T OTA, assume the input pair is biased at a given g_m/I_D . Achieving higher ____ necessitates higher power consumption.

A	CMRR	B	Gain	C	BW	D	GBW
---	------	---	------	---	----	---	-----

$$GBW = \frac{g_{m1,2}}{2\pi C_L} \rightarrow \text{for a given } \frac{g_m}{I_D} \text{ the higher } I_D \rightarrow \text{the higher } g_m \rightarrow \text{the higher GBW}$$

10. For the shown 5T OTA, if there is a strict spec on the fanout ($FO = C_L/C_{in}$), i.e., a small C_{in} is required, then the following assumption should be used to satisfy the gain spec: _____.

A	$r_{o2} \ll r_{o4}$	B	$r_{o2} \gg r_{o4}$	C	$r_{o2} = r_{o4}$	D	All answers are wrong
---	---------------------	---	---------------------	---	-------------------	---	-----------------------

$$\text{Smaller } C_{in} \rightarrow \text{Smaller Area of input devices} \rightarrow \text{Smaller L for input device} \rightarrow r_{o2} \ll r_{o4}$$