


1. For the cascode amplifier below, assume all transistors have the same g_m and the same r_o . If for all transistors $V_A = 10$ V and $V_{ov} = 140$ mV, then the voltage gain in dB ($20 \cdot \log|A_v|$) is approximately equal to _____ dB.

$$1 \quad A_v = G_m R_{out}$$

$$2 \quad G_m = g_m \quad \text{and} \quad R_{out} = g_m r_o^2 \cdot \frac{1}{2}$$

$$3 \quad A_v = (g_m r_o)^2 \cdot \frac{1}{2} = \left(\frac{2I_D}{V_{ov}} \cdot \frac{V_A}{I_D} \right)^2 \cdot \frac{1}{2} = \left(\frac{2V_A}{V_{ov}} \right)^2 \cdot \frac{1}{2}$$
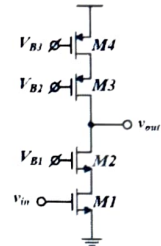
$$4 \quad A_v = 10204 \text{ V/V} \approx 80 \text{ dB}$$




2. For the shown cascode amplifier, if V_{out} decrease below its minimum value, the first transistor to come out of saturation (enter triode) is _____.

∞ V_{DS1} is defined by the strong voltage V_B

∞ When V_{out} decrease, V_{DS2} decrease

∞ M2 is the first

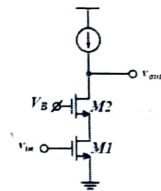

3. The cascode amplifier boosts the gain compared to a simple CS amplifier by boosting _____.


A	<input checked="" type="checkbox"/> R_{out}	B	<input type="checkbox"/> G_m	C	<input type="checkbox"/> R_{in}	D	<input type="checkbox"/> G_m and R_{out}
---	---	---	--------------------------------	---	-----------------------------------	---	--

4. For the shown regulated cascode amplifier, assume all transistors have the same V_{TH} and V_{ov} . The maximum output swing is achieved when V_{B2} is set to less than _____.

max output swing is 2 V_{ov} $V_{out} = 2V_{ov}$

∞ M1 needs $V_{DS} = V_{ov}$ at least
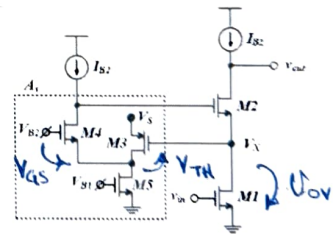
$$\begin{aligned} \infty \quad V_{B2} &= V_{GS} + V_{TH} + V_{ov} \\ &= 2V_{TH} + 2V_{ov} \end{aligned}$$




5. You are required to design an NMOS cascode that has $R_x = 500$ k ohm and $I_D = 0.5$ mA. What is the W/L that you are going to use?

Assume $\mu \cdot C_{ox} = 400$ $\mu\text{A/V}^2$, $V_A = 10$ V, and M1 and M2 are identical.

$$1 \quad R_x = g_m r_o^2 = \frac{2I_D}{V_{ov}} \cdot \left(\frac{V_A}{I_D} \right)^2 = 500 \text{ k}\Omega$$

$$2 \quad V_{ov} = 0.8 \text{ V}$$

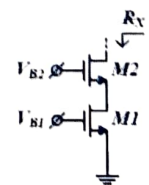
$$3 \quad I_D = \frac{\mu C_{ox}}{2} \frac{W}{L} \cdot V_{ov}^2 = 0.5 \text{ mA} \rightarrow \frac{W}{L} = 3.9$$



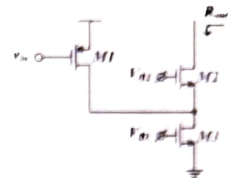6. Assume all transistors have the same V_{ov} and same V_A , and M1 and M2 have the same bias current (hint: what is the current in M3?). R_{out} is approximately equal to $g_{m2} \cdot r_{o2}^2 / a$ where 'a' is equal to _____


Hint: r_o depends on both V_A and I_D .

$$\begin{aligned} 1 & \text{ M1 and M2 have same } I_D \rightarrow \text{M3 has } 2I_D \\ 2 & r_{o3} = \frac{1}{2} r_{o1,2} \\ 3 & R_{out} = r_{o1,2} g_{m2} \cdot \left(\frac{1}{2} r_{o1,2} \parallel r_{o1,2} \right) = \frac{1}{3} g_{m2} r_{o1,2}^2 \end{aligned}$$



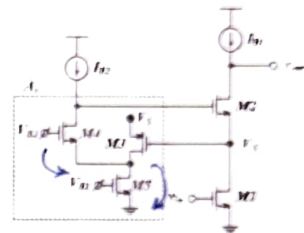
7. For the shown regulated cascode amplifier, assume all transistors have the same V_{TH} and V_{ov} . The minimum valid value for V_{B2} is equal to _____.

$$\begin{aligned} V_{B2min} &= V_{GS} + V_{ov} = V_{TH} + V_{ov} + V_{ov} \\ &= V_{TH} + 2V_{ov} \end{aligned}$$



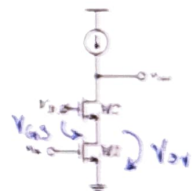
8. For the shown cascode amplifier, assume M1 and M2 have the same V_{TH} and V_{ov} . The maximum output swing is achieved when V_B is set to _____.

$$\begin{aligned} \text{max swing @ } V_{outmin} &= 2V_{ov} \\ \therefore V_B &= V_{GS} + V_{ov} = V_{TH} + 2V_{ov} \end{aligned}$$



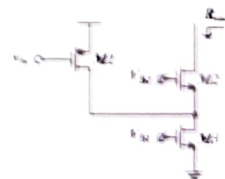9. Assume all transistors have the same g_m and same r_o . R_{out} is approximately equal to $g_{m2} \cdot r_{o2}^2 \cdot a$ where 'a' is equal to _____

$$\begin{aligned} 1 & R_{out} = g_{m2} r_{o2} (r_{o3} \parallel r_{o1}) \\ 2 & \text{ If all transistors have the same } g_m \text{ and } r_o \\ 3 & R_{out} = g_m r_o^2 \cdot \frac{1}{2} \end{aligned}$$



10. Assume the following:

M1 and M3 have the same bias current (hint: what is the current in M2?)

M2, M3, M4, and M5 have the same V_A (Hint: what is the relation between their r_o ?)

M3 and M4 have the same g_m (hint: do we need g_{m2} and g_{m5} to calculate the gain?)

$$g_{m1} = 2 * g_{m3}$$

$$r_{o1} = r_{o3} / 4$$

The gain is approximately equal to $a * (g_{m3} * r_{o3})^2$ where 'a' is equal to _____.

$$\begin{aligned} 1 \quad A_v &= G_m R_{out} \\ 2 \quad G_m &= g_{m1} = 2 g_{m3} \\ 3 \quad R_{out} &= g_{m4} r_{o4} r_{o5} \parallel g_{m3} r_{o3} (r_{o2} \parallel r_{o1}) \\ &= g_{m3} r_{o3}^2 \parallel g_{m3} r_{o3} \left(\frac{1}{2} r_{o3} \parallel \frac{1}{4} r_{o3} \right) \\ &= g_{m3} \left(r_{o3}^2 \parallel \frac{1}{6} r_{o3}^2 \right) = g_{m3} r_{o3}^2 \cdot \frac{1}{F} \\ 4 \quad A_v &= \frac{2}{F} (g_{m3} r_{o3})^2 = 0.29 (g_{m3} r_{o3})^2 \end{aligned}$$

