

① The dominant pole in the HFR is usually caused by high impedance node

② Consider IC CS amp with

$$R_{sig} = 20k, R_{eff} = \frac{r_o}{2} = 10k\Omega, g_m = 4mS, C_{gs} = 20fF$$

$$C_{gd} = 2fF, C_{sb} = C_{db} = 10fF \text{ and } C_L = 15fF$$

$$\therefore f_c = \frac{\omega_c}{2\pi} \text{ is approx. equal to}$$

$$f_c = \frac{g_m}{2\pi C_{gd}} \approx 320 \text{ GHz.}$$

③ If the output pole of the amplifier is the dominant pole, then increasing  $R_{out}$  will ... the GBW of the amp

$$GBW = A_v \cdot BW = g_m R_{out} \cdot \frac{1}{2\pi C_{out} R_{out}} \neq f(R_{out})$$

$\therefore$  Not change

④ If a capacitance  $C_F$  is connected between the input and the output of a buffer, the effective input cap is ...  $C_F$

⑤ If both designed under the same conditions, the BW of CG amplifier is higher than the BW of CS amplifier because ... CG amplifier does not suffer from miller effect

⑥ For a CG amplifier, the dominant pole is usually the ... output pole

⑦ The Cascode amplifier with  $R_D \ll r_o$  can provide ... bandwidth compared to a CS amplifier that has the same load resistance higher

⑧ for a CS amplifier, the dominant pole is usually the -- Pole  
Input

⑨ Consider a Common Gate amplifier,  $g_m = 4 \text{ mS}$ ,  $r_o$  is very large  
 $C_{gs} = 20 \text{ fF}$ ,  $C_{gd} = 5 \text{ fF}$ ,  $C_{sb} = C_{db} = 10 \text{ fF}$ ,  $C_L = 15 \text{ fF}$   
 $R_{sig} = 10 \text{ k}\Omega$  and  $R_L = 10 \text{ k}\Omega$ . The dominant pole frequency  
is approximately equal to --

$$\omega_{pd} = \frac{1}{2\pi R_L (C_L + C_{db} + C_{gd})} = 530 \text{ MHz}$$

⑩ Consider an IC CS amplifier fed with a source having  
source resistance  $R_{sig} = 20 \text{ k}\Omega$  and having an effective load  
resistance  $R_L$  composed of  $r_o$  of the transistor parallel with  
equal  $r_o$  of current source load.

$g_m = 4 \text{ mS}$ ,  $r_o = 20 \text{ k}\Omega$ ,  $C_{gs} = 20 \text{ fF}$ ,  $C_{gd} = 2 \text{ fF}$ ,  $C_{sb} = C_{db} = 10 \text{ fF}$   
 $C_L = 15 \text{ fF}$ . the dominant pole frequency is approx equal to --

$$\omega_{pd} = \frac{1}{2\pi R_{sig} (C_{gd} * A_v + C_{gs})}$$

$$A_v = g_m \frac{r_o}{2} = 40$$

$$\therefore \omega_{pd} = 80 \text{ MHz}$$