

## Quiz: Frequency Response (1)

① A pole Causes a total Phase shift equal to --

- 90 degrees

② For  $H(s) = \frac{10s(1+s)(1-\frac{s}{10^9})}{(1+\frac{s}{10^2})^2(1+\frac{s}{10^6})(1+\frac{s}{10^9})}$  the Phase

shift is equal to --

∴ No. of zeros = 3  $\begin{cases} \nearrow 2 \text{ in LHP} \rightarrow -180^\circ \\ \searrow 1 \text{ in RHP} \rightarrow +90^\circ \end{cases}$

∴ No. of Poles = 4 (All in LHP)  $\rightarrow -360^\circ$

∴ at Very high freq. Phase shift =  $-270^\circ$

③ For  $H(s) = \frac{10s}{(1+\frac{s}{10^2})(1+\frac{s}{10^7})}$ , the Phase at  $\omega = 2 \times 10^4$  rad/s is approx. equal to --

$$\therefore H(j\omega) = \frac{10 \times 2 \times 10^4 j}{(2 \times 10^2 j)(1)} = 10^3$$

∴ Phase =  $0^\circ$

④ For a CS amplifier with degeneration resistance shunted by a bypass Cap, the bypass Cap acts as --  
HPF

⑤ A RHP zero Causes a total Phase shift that is equal to --

- 90 degree

⑥ for a CS amplifier, the feed forward zero is caused by  $C_{gd}$ , lies on

$$\omega_{\infty} S_{\alpha} = -\frac{G_m}{C_F} \quad \text{and } G_m \text{ for CS is } -g_m$$

$$\therefore S_{\alpha} \text{ is } +g_m \rightarrow \infty \text{ in RHP}$$

⑦ for  $H(s) = \frac{10^3}{(1 + \frac{s}{10^2})(1 + \frac{s}{10^7})}$ , the midband gain is equal to  $\dots$  dB

$$\omega \gg 10^2 \text{ and } \omega \ll 10^7$$

$$\therefore H(j\omega) = \frac{10^3}{(\frac{j\omega}{10^2})(1)} = 10^3 = 60 \text{ dB}$$

⑧ The  $\omega_{TC}$  technique gives an estimate for the dominant pole in the high-freq range.  
Pessimistic

⑨ for  $H(s) = \frac{s^2(1 - \frac{s}{10^6})}{(1+s)^2(1 + \frac{s}{10^3})(1 + \frac{s}{10^9})}$  the magnitude

at  $\omega = 5 \times 10^7$  rad/s is approx equal to  $\dots$  dB

$$H(j\omega) = \frac{-(5 \times 10^7)^2 (-5 \times 10^6)}{-(5 \times 10^7)^2 (5 \times 10^4 j)(1)} = \frac{1}{10^3 j}$$

$$\therefore |H(j\omega)| = -60 \text{ dB}$$

⑩ for MOS biased in pinch-off, the largest cap is  $C_{gs}$