


1.

The dual-supply op-amp below is connected in a negative feedback configuration as a non-inverting amplifier. Assume $V_{in} = 1V$, the op-amp open-loop DC gain $A_{OL} = 1000$, $R_1 = 5\text{ k}\Omega$ and $R_2 = 1\text{ k}\Omega$.

The first stage of the op-amp is a differential amplifier.

The differential input voltage of the differential amplifier is equal to _____ mV.

Hint: Do NOT assume $LG \gg 1$.

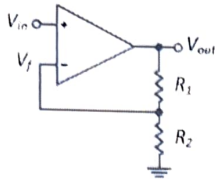

$$V_{id} = \frac{V_{out}}{A_{OL}} = \frac{V_{in} A_{cl}}{A_{OL}}$$


$$\therefore A_{cl} = \frac{A_{OL}}{1 + \beta A_{OL}} = \frac{1000}{1 + \frac{1}{6} \cdot 1000} = 5.96$$

$$\therefore V_{id} = \frac{5.96}{1000} = 5.96\text{ mV}$$

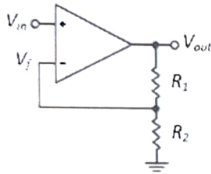2.

The op-amp below is connected in a negative feedback configuration as a non-inverting amplifier. Assume $V_{in} = 1V$, the op-amp open-loop DC gain $A_{OL} = 1000$, $R_1 = 2\text{ k}\Omega$ and $R_2 = 1\text{ k}\Omega$.

The static gain error (in percent) is equal to _____ %.



$$E_s = \frac{|A_{cl, \text{actual}} - A_{cl, \text{ideal}}|}{A_{cl, \text{ideal}}} \times 100$$

$$\therefore A_{cl, \text{ideal}} = \frac{1}{\beta} = \frac{1}{3}, \quad A_{cl, \text{actual}} = \frac{1000}{1 + \frac{1000}{3}} = 2.991$$

$$\therefore E_s = 0.299\%$$

3.


For a feedback system, the unity-gain frequency of the _____ depends on the feedback factor (β).



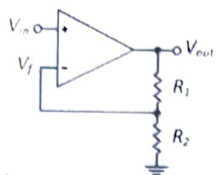4.

The op-amp below is connected in a negative feedback configuration as a non-inverting amplifier. Assume $V_{in} = 1V$, the op-amp open-loop DC gain $A_{OL} = 1000$, the op-amp open-loop bandwidth $BW_{OL} = 100\text{ Hz}$, $R_1 = 4\text{ k}\Omega$ and $R_2 = 1\text{ k}\Omega$.


The closed loop bandwidth of the amplifier is equal to _____ kHz.



$$\begin{aligned} BW_{cl} &= BW_{OL} \cdot (1 + \beta A_{OL}) \\ &= 100 \times \left(1 + \frac{1000}{5}\right) \\ &= 20.1\text{ kHz} \end{aligned}$$

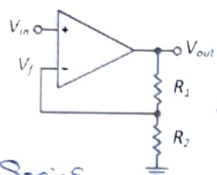5.

The feedback type in the amplifier below is _____.



Series
mixing

Shunt Sensing

series mixing - shunt sensing

6.

The following systems always have a large phase margin (select all correct answers):

1st order


7.

The dual-supply op-amp below is connected in a negative feedback configuration as a non-inverting amplifier. Assume $V_{in} = 1V$, the op-amp open-loop DC gain $A_{OLO} = 1000$, $R_1 = 4\text{ k}\Omega$ and $R_2 = 1\text{ k}\Omega$.

The exact voltage at the (-) terminal of the op-amp is equal to

Hint: Do NOT assume $LG \gg 1$ when you calculate the exact voltage.

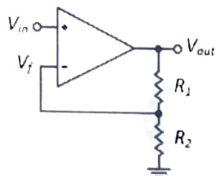Note: Write the answer with 3 decimal places (three digits after the decimal point), e.g. 1.211.



$$V_f = V_{out} \times \beta = V_{in} A_{OL} \times \beta$$

$$= 1 \cdot \frac{1000}{1 + \frac{1000}{5}} \times \frac{1}{5} = 0.995$$

8.

For an OTA connected as negative feedback amplifier, if the input signal experiences large transient steps, the optimum ratio between the non-dominant pole and the UGF is


4

9.

The op-amp below is connected in a negative feedback configuration as a non-inverting amplifier. Assume $V_{in} = 1V$, the op-amp open-loop DC gain $A_{OLO} = 1000$, $R_1 = 3\text{ k}\Omega$ and $R_2 = 1\text{ k}\Omega$.

The first stage of the op-amp is a differential amplifier.

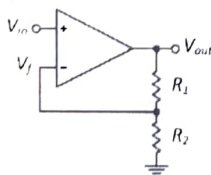The CM input voltage of the differential amplifier is approximately equal to ... V.



$$V_f = V_{out} \times \beta = 1 \cdot \frac{1000}{1 + \frac{1000}{4}} \cdot \frac{1}{4} = 0.996V$$


$$V_{CM} = \frac{V_+ + V_-}{2} = 0.998V$$

10.

The op-amp below is connected in a negative feedback configuration as a non-inverting amplifier. Assume $V_{in} = 1V$, the op-amp open loop DC gain $A_{OL} = 1000$, $R_1 = 4\text{ k}\Omega$ and $R_2 = 1\text{ k}\Omega$.

The closed loop time constant of the amplifier is required to be $100\text{ }\mu\text{s}$.

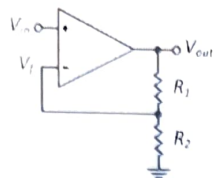The op-amp should be designed such that the open-loop bandwidth is equal to _____ Hz.



$$BW_{CL} = \frac{1}{2\pi \tau_{cl}} = \frac{1}{2\pi \cdot 100\mu} = 1.591\text{ kHz}$$

$$BW_{OL} = \frac{BW_{CL}}{1 + \beta A_{OL}} = 7.918\text{ Hz}$$