

# Analog Integrated Systems Design


## Lecture 11 Comparators

**Dr. Hesham A. Omran**


Integrated Circuits Laboratory (ICL)  
Electronics and Communications Eng. Dept.  
Faculty of Engineering  
Ain Shams University
 
# Comparator

- ❑ The comparator circuit is the location where the digital decision is made
  - “Where nature turns into bits”
- ❑ Detects the polarity of a differential analog input signal
  - Generates a digital output (1 or 0) accordingly
- ❑ Or compares a SE input to a threshold (reference) voltage
  - Threshold-crossing detector




Circuit symbol

 

Transfer characteristic  
(ideal)
 
# Comparators in ADCs

- ❑ Every analog-to-digital converter contains at least one comparator
- ❑ There are many different comparator implementations
  - There is NO universal “one design fits all” comparator
- ❑ Main design trade-off: accuracy and speed vs power consumption




# Comparator Requirements

- ☐ Large amplification (fine resolution / high sensitivity)
  - Needs to translate mV or uV differential input to '0' and '1'
- ☐ Wide bandwidth (high speed)
- ☐ Accuracy
  - Low input offset and low noise
- ☐ Low power consumption
- ☐ No memory (hysteresis)
  - Previous comparator decision should not affect the following
- ☐ No metastability
  - Any decision is better than no decision!
- ☐ Wide common mode input range
- ☐ High CMRR

# Comparator Topologies


- ❑ Straight-forward amplification

- Simple
- Relatively slow

 

 
## ❑ Latch comparator

- **A.k.a. clocked / dynamic / regenerative comparator**
- **Clock is required**
- **Built-in S/H**




 
# Pre-amplification

- ❑ A pre-amplifier is used before the regenerative section of the comparator is activated
  - Reduces the influence of mismatch in the regenerative section
  - Creates a form of isolation between the regeneration process and the input sources
  - No reason to boost the DC-gain to very high values (usually  $\leq 10$ )
    - Low gain allows operations at high speed (large bandwidth)
    - Just sufficient to suppress latch mismatch and noise
- ❑ Most comparators use an input differential pair as a pre-amplifier



  
# Regenerative Comparator Example

- ❑ After some amplification a positive feedback latch activated by a clock pulse will turn the latch on
  - The latch will amplify the small input voltage difference to a large signal



# Regenerative Latch Delay

 





# Regenerative Latch Delay

- Assume the pre-amplified latch input voltage =  $\Delta V_{in} = \alpha V_{LSB}$  ( $0 < \alpha < 1$ )

$$\tau \approx \frac{C}{g_{m,l}}$$

$$V(t) = \Delta V_{in} e^{+t/\tau}$$

  
- The exponential signal growth makes a latch a fast decision element in a regenerative comparator
- The exponential growth will continue until some non-linear limiting mechanism takes action (e.g., approaching power rails)


 
# Comparator Delay Example


- ❑ The time a comparator or latch needs to form a digital signal depends on the initial over-drive voltage
  - The input differential voltage determines the delay of the comparator

$$V(t) = \Delta V_{in} e^{+t/\tau} \rightarrow t_d = \tau \ln \frac{V_{FS}}{\Delta V_{in}} = \tau (\ln V_{FS} - \ln \Delta V_{in})$$


 
# Metastability

- ❑ For very small overdrive voltages, the comparator cannot reach a decision in the limited time of a clock period ( $T_S$ )
- ❑ The comparator will not generate a clear “zero” or “one” output level after time  $T_S$
- ❑ The succeeding logical circuitry will behave ambiguously



# Bit-Error Rate (BER)

- ❑ Assume the pre-amplified latch input voltage =  $\alpha V_{LSB}$  ( $0 < \alpha < 1$ )
- ❑ Assume ambiguity happens when  $V(T_S) < V_{FS}$

$$V(T_S) = \alpha V_{LSB} e^{+T_S/\tau} < V_{FS}$$

$$\alpha_{min} = \frac{V_{FS}}{V_{LSB}} e^{-T_S/\tau} = 2^N e^{-T_S/\tau}$$

- ❑ Assume  $V_{in}$  is uniformly distributed:  $0 < \alpha < 1$

$$BER = \alpha_{min} = 2^N e^{-T_S/\tau}$$

# Bit-Error Rate (BER)

- Assume  $V_{in}$  is uniformly distributed:  $0 < \alpha < 1$

$$BER = \alpha_{min} = 2^N e^{-T_s/\tau}$$

- From a fundamental point of view the BER cannot be avoided completely
  - But can be made very small ( $10^{-13}$  is possible)
- Measures to improve the BER include:
  - Improving the latch speed with more current and smaller capacitances
  - Additional gain stages or a second latch
    - $\Delta V_{in} = \alpha V_{LSB}$  larger than  $V_{LSB}$  ( $0 < \alpha < A$ , where  $A > 1$ )
  - Using special decoding scheme to avoid large code errors in case of a metastable state


# Comparator Offset Voltage

- ❑ In some types of ADCs the static random offset just generates a (random) DC-shift of the entire signal → offset error
- ❑ In other types of ADCs the input referred random offset is crucial because it impacts both INL and DNL
  - $0.5\text{LSB} > 3\sigma_{in,os}$


# Static vs Dynamic Offset

- ❑ Offset voltage has static and dynamic components
  - Static offset:
    1. Systematic offset (due to systematic mismatch): can be minimized by good design and matched layout
    2. Random offset (due to random mismatch): reduced by using large devices but cannot be eliminated (Pelgrom's model)
      - Static offset is dominant in preamplifiers
  - Dynamic offset:
    - Due to imbalanced switching effects and capacitive load mismatch
    - Dynamic offset is dominant in latches

# Multistage Preamplifier Offset

 

Individual stage

 


Total input-referred

$$A_T = A_1 \cdot A_2 \cdot A_3$$
$$V_{os} = V_{os1} + \frac{V_{os2}}{A_1} + \frac{V_{os3}}{A_1 \cdot A_2}$$



 
# Comparator Static Offset

$$\sigma_{V_{in}}^2 = \sigma_{V_{T,12}}^2 + \frac{g_{m,34}^2}{g_{m,12}^2} \sigma_{V_{T,34}}^2 + \frac{I_{load}^2}{g_{m,12}^2} \frac{\sigma_R^2}{R_{1,2}^2}$$



 
# Latch Dynamic Offset

- ❑ M5-6: input pair
- ❑ M7-8: cross-coupled load (regenerative)
- ❑ M9: reset switch
  
- ❑ Dynamic offset due to:
  - Imbalanced CI and CF
  - Imbalanced load capacitance
  - Mismatch between  $M_5$  and  $M_6$
  - Mismatch between  $M_7$  and  $M_8$
  - Clock routing



 
# Input Offset Cancellation

- ❑ AC coupling at input with input-referred offset stored in C
- ❑ Two-phase operation
  - Phase ( $\Phi_2$ ) is used to store offset


 
# Input Offset Cancellation


- ❑ Offset Storage Phase –  $\Phi_2$ 
  - Closed-loop stability required (amplifier in unity-gain feedback)



Ref: J. L. McCreary and P. R. Gray, "All-MOS charge redistribution analog-to-digital conversion techniques. I," *JSSC*, vol. 10, pp. 371-379, issue 6, 1975.
 
# Input Offset Cancellation

- Amplifying Phase –  $\Phi_1$ 
  - Offset cancellation is incomplete if  $A$  is finite
  - Input AC coupling attenuates signal gain





$$\begin{aligned} V_o &= -A(V_{in} + V_c - V_{os}) \\ &= -A\left(V_{in} - \frac{V_{os}}{1+A}\right) \end{aligned}$$

Input - referred offset :

$$V_{os,in} = \frac{V_{os}}{1+A}$$

  
# Input Offset Cancellation

- Fully differential operation to mitigate charge injection and clock feedthrough errors.
  - Necessary for any high precision switched-capacitor integrated circuits



 
# Output Offset Cancellation

- ❑ AC coupling at output with offset stored in C
- ❑ The gain (A) must be small and stable (independent of  $V_o$ )
- ❑ Does not work for high-gain amplifier


 
# Output Offset Cancellation

- ❑ Offset Storage –  $\Phi_2$ 
  - Closed-loop stability is not required
  - CF (clock feedthrough) and CI (charge injection) of  $\Phi_2'$  gets divided by  $A$  when referred to input




Ref: R. Poujois and J. Borel, "A low drift fully integrated MOSFET operational amplifier," JSSC, vol. 13, pp. 499-503, issue 4, 1978.



# Output Offset Cancellation
 
## □ Amplifying Phase – $\Phi_1$

- Cancellation is complete if  $A$  is constant (independent of  $V_o$ )
- AC coupling at output attenuates signal gain



$$\begin{aligned} V_o &= A(V_i - V_{os}) + AV_{os} \\ &= AV_{in} \end{aligned}$$



Input-referred offset:


$$V_{os,in} = 0$$

# Comparator Noise

- ❑ The input referred noise voltage acts as time varying input offset
- ❑ If the thermal noise dominates:


$$v_{nout,rms}^2 = v_{nin}^2(f) \times A_v^2 \times B_N = \frac{4kT\gamma_{eff}}{g_m} \times A_v^2 \times B_N$$
$$v_{nin,rms} = \sqrt{\frac{4kT\gamma_{eff}}{g_m} \times B_N}$$

 - ❑ Trade-off between noise, speed, and power consumption



 
# Quiz: Offset and Noise

- Calculate the offset and noise from the shown measured comparator characteristics.



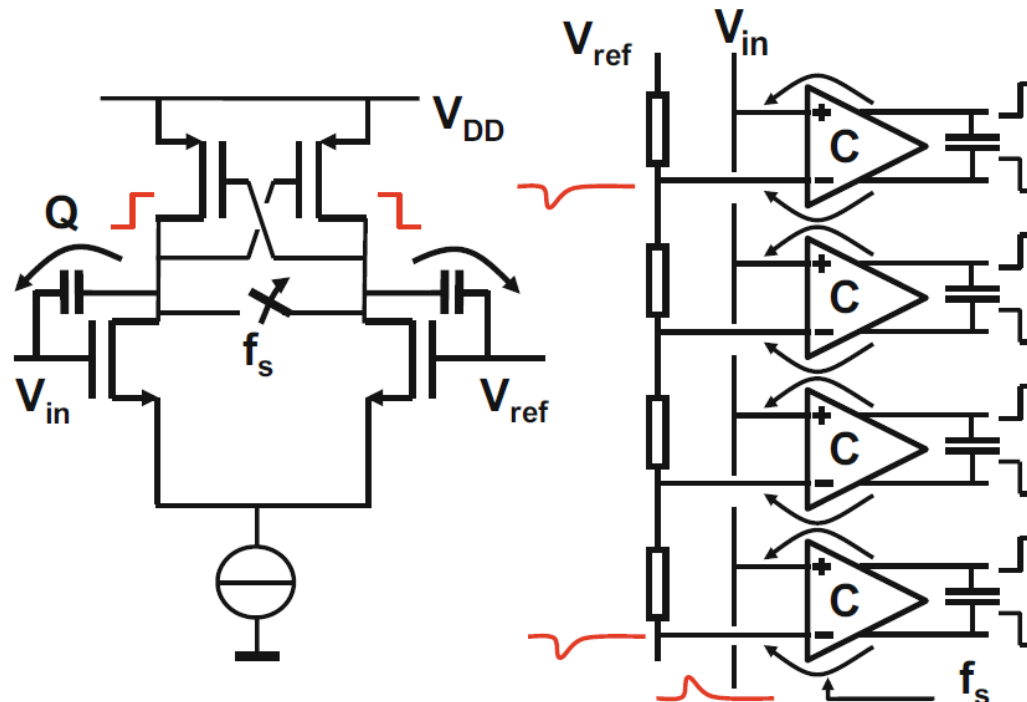
# Kickback Noise

- ❑ The output has sharp voltage transitions
- ❑  $C_{gd}$  will pass these fast edges to  $V_{in}$  and  $V_{ref}$  causing “kickback”
  - Reference voltage disturbance must settle before next sample
- ❑ Reducing  $C_{gd}$  by reducing sizing will make mismatch worse
- ❑ The output swing can be reduced by using limiting circuits



 
# Hysteresis

- ❑ Hysteresis: the comparator remembers its previous state.
- ❑ Either intentionally or as an unwanted consequence of the topology.
- ❑ Schmitt-trigger comparators use the hysteresis threshold to avoid unwanted transitions in case of noise signals
- ❑ The resolution of the comparator can be no less than the hysteresis
  - Large values of hysteresis are generally BAD for a high resolution comparator



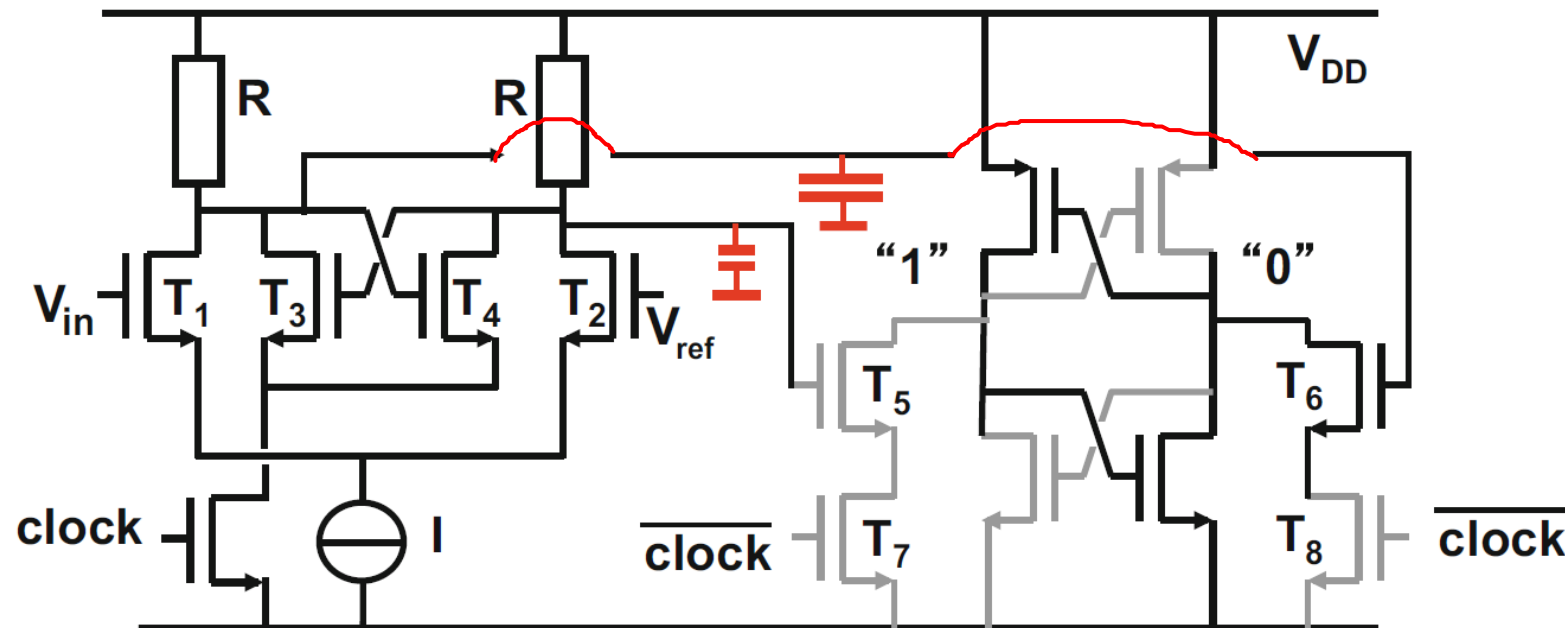
# Hysteresis Example

- ❑ A pre-latch stage that is connected to a second stage consisting of a full digital latch activated by the inverse clock
- ❑ For the example below: ON transistor (T6) has much higher capacitance than T5
- ❑ The unequal capacitive loading favors a similar signal in the first latch → The consequence is a comparator with hysteresis.



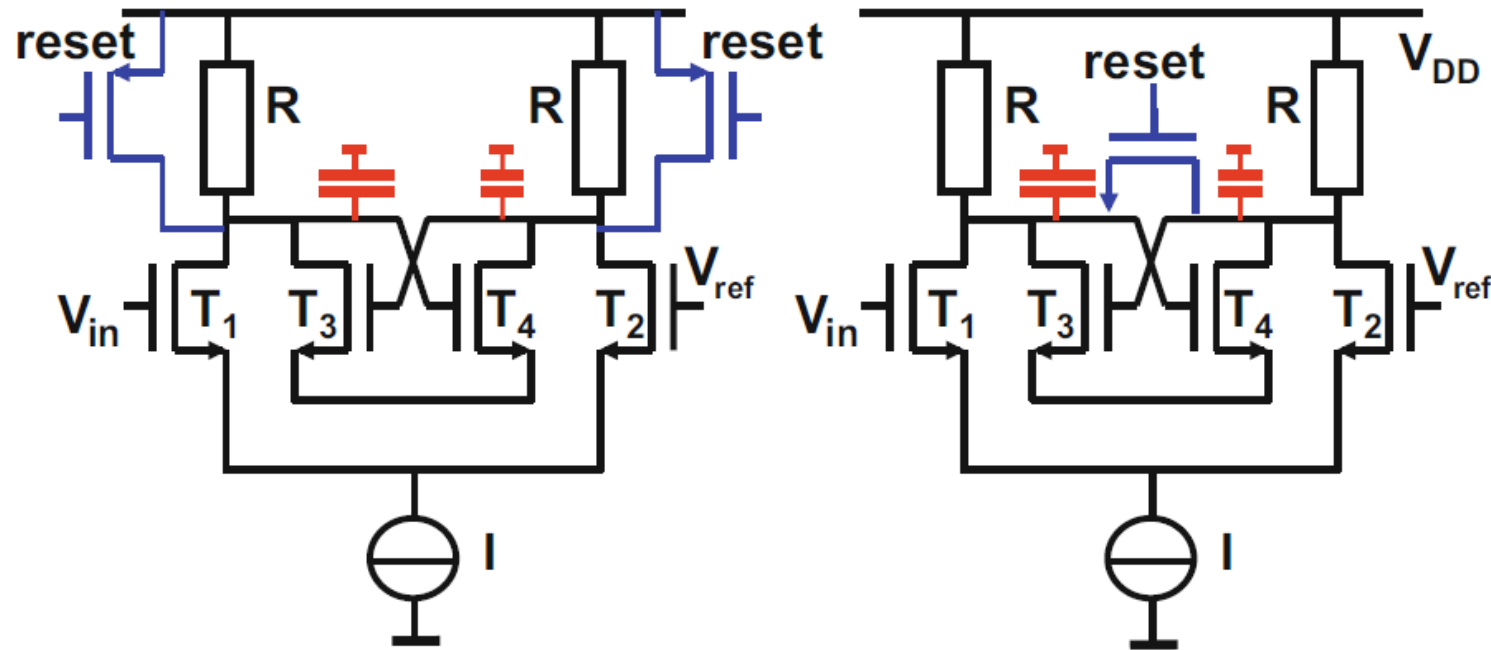
# Removing Hysteresis

- ❑ The previous state can be removed by resetting the latch in the comparator




# Overdrive Recovery Test

- ❑ A small input ( $\pm 0.5$  LSB) is applied to the comparator input in a cycle right after a full-scale input is applied
  - The comparator should be able to resolve to the right output in either case  $\rightarrow$  memoryless

 

Case I

 


Case II






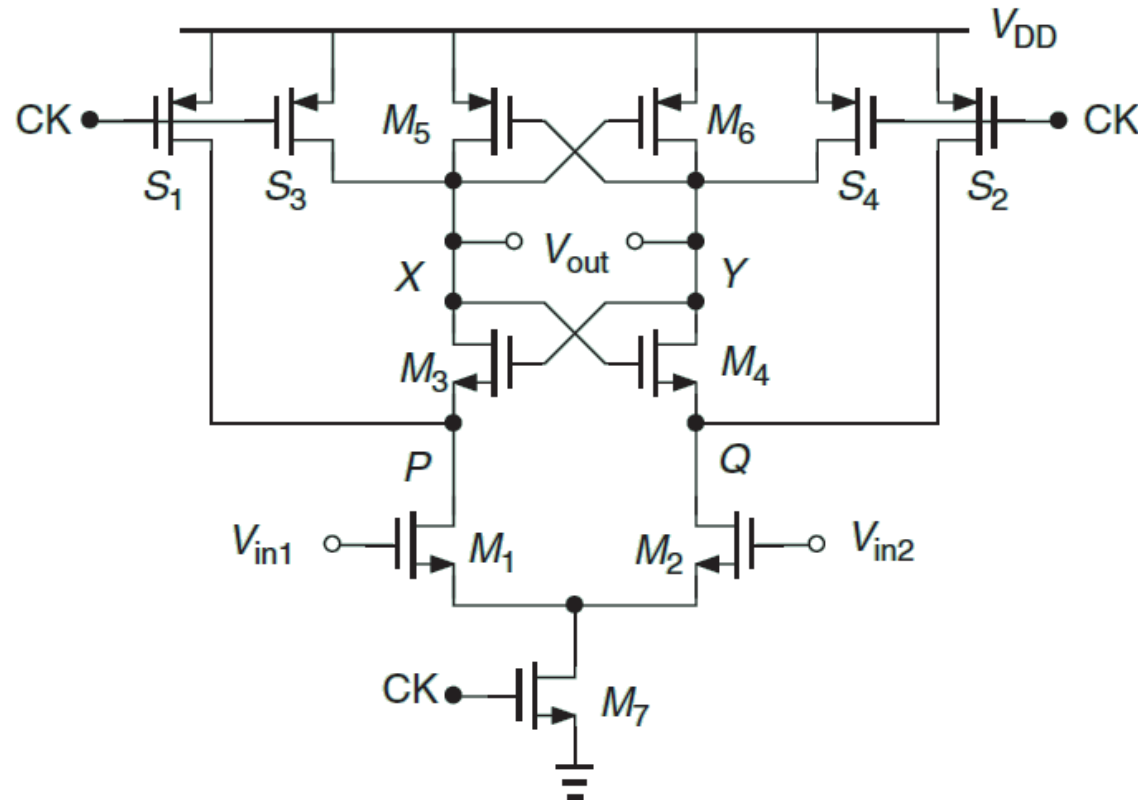
# The StrongArm Latch

- ❑ A popular latch design used in the StrongARM MPU in the 1990s
  - The input offset is relatively large (pre-amp or calib required)
  - Many modified versions exist



  
 
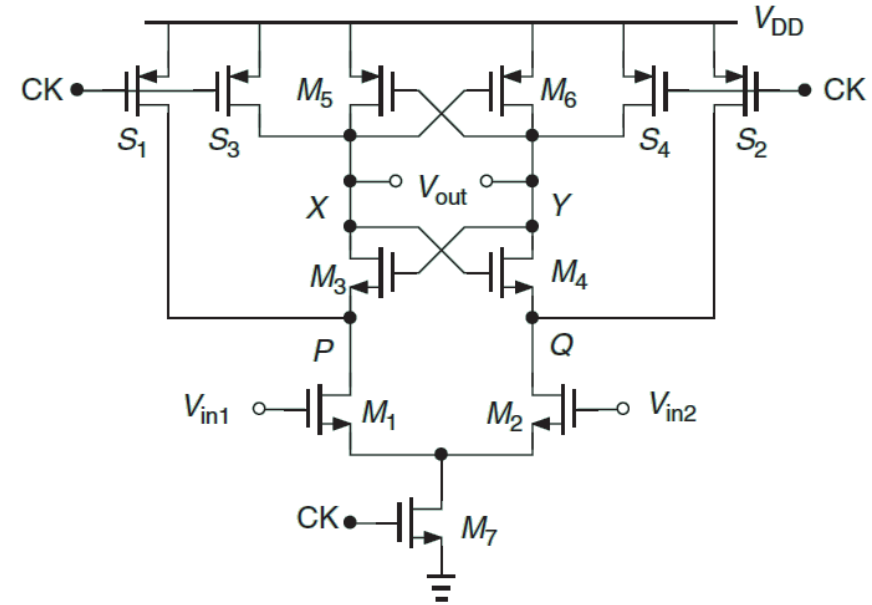
# The StrongArm Latch

- ❑ Precharge phase:  $CK = 0$
- ❑ S1-4
  - Reset the latch and remove previous states (hysteresis)
  - Keep M3-6 initially off reducing their offset contribution
- ❑ Amplification phase:  $CK = 1$



 
 
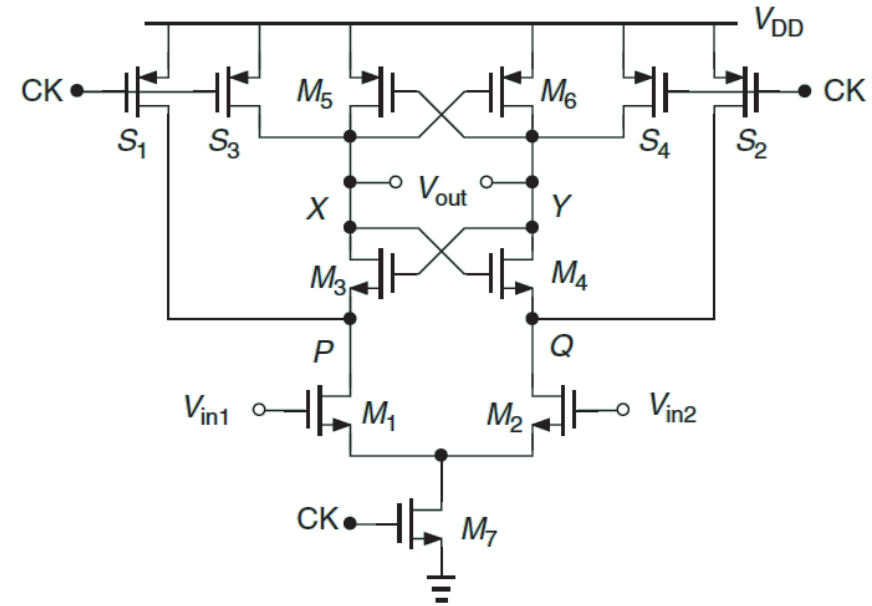
# The StrongArm Latch

- ❑ NMOS cross-coupled pair (M3,4) turns on
- ❑ M3,4 and M5,6 act as cross-coupled CMOS inverters
  - No static current flows



   
# The StrongArm Latch

- ❑ PMOS cross-coupled pair (M5,6) turns on
- ❑ Positive feedback brings one node to VDD and the other to GND





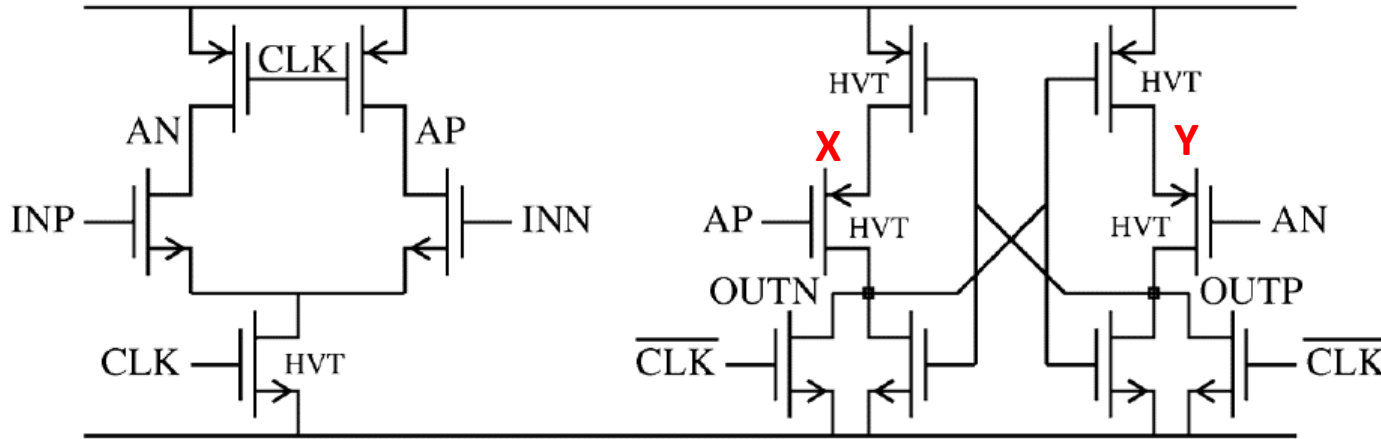
# Fast Low-leakage Dynamic Comparator

- ❑ Comparator for low-power 8-bit SAR ADC (LSB = 3.2mV)



PMOS: 2.5u/0.1u  
NMOS: 8u/0.4u (Diff. pair), 2.5u/0.2u (Tail switch)

PMOS: 2u/0.2u  
NMOS: 0.4u/0.1u

   

# References

- ❑ M. Pelgrom, Analog-to-Digital Conversion, Springer, 3<sup>rd</sup> ed., 2017.
- ❑ W. Kester, The Data Conversion Handbook, ADI, Newnes, 2005.
- ❑ T. C. Carusone, D. Johns, and K. W. Martin, “Analog Integrated Circuit Design,” Wiley, 2<sup>nd</sup> ed., 2012.
- ❑ B. Boser and H. Khorramabadi, EECS 247 (previously EECS 240), Berkeley.
- ❑ B. Murmann, EE 315, Stanford.
- ❑ Y. Chiu, EECT 7327, UTD.

---

**Thank you!**