

Analog Integrated Circuits.

Page 8

Lect 8 Noise Fundamentals.

① Noise in time domain.

- noise is unwanted random signal.
- We cannot predict (model) its instantaneous value
- But we can predict (model) noise statistical dis.

② Noise statistical distribution.

- Noise has normal (gaussian) distribution.
- the mean = 0 \rightarrow avg noise voltage in time domain = 0
- the Variance (σ^2) is the mean-square value
- the standard deviation (σ) is the r.m.s value.
- usually, Peak to Peak instantaneous noise voltage is within $\pm 3\sigma$

③ Noise Power and noise voltage

* The avg Power of a periodic sig. $\rightarrow P_{avg} = \frac{1}{T} \int_{-T/2}^{T/2} P(t) dt = \frac{1}{T} \int_{-T/2}^{T/2} \frac{V^2(t)}{R_L} dt$

$= \frac{1}{R_L} \cdot \frac{1}{T} \int_{-T/2}^{T/2} \overset{\text{Square}}{V_n^2(t)} dt = \frac{\overset{\text{mean-square/Varianc}}{\overline{V_n^2}}}{R_L} = \frac{\sigma_n^2}{R_L}$

* The avg Power of a non-periodic sig. $\rightarrow P_{avg} = \frac{1}{R_L} \cdot \lim_{T \rightarrow \infty} \frac{1}{T} \int_{-T/2}^{T/2} V_n^2(t) dt = \frac{\overline{V_n^2}}{R_L} = \frac{\sigma_n^2}{R_L}$

* The mean-square noise voltage $\rightarrow \overline{V_n^2} = \lim_{T \rightarrow \infty} \frac{1}{T} \int_{-T/2}^{T/2} V_n^2(t) dt = \sigma_n^2 \propto P_{avg}$


* The root-mean-square of noise voltage $\rightarrow V_{n,rms} = \sqrt{\overline{V_n^2}} = \sigma_n$

④ Noise in frequency domain.

- a signal $x(t)$ has Power spectral density (PSD) $= S_x(f)$

↳ how much power is carried around each frequency.

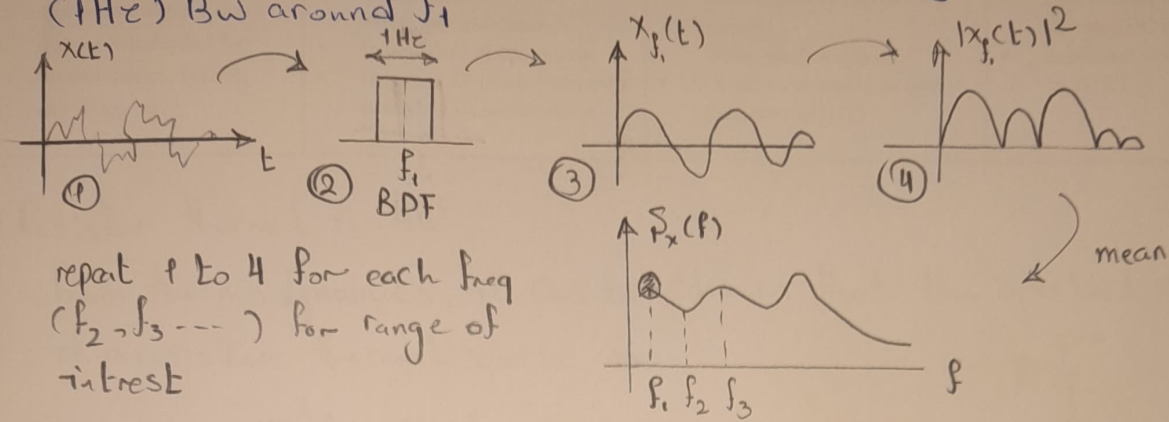- PSD of a noise signal $x(t)$ at freq f_1 is the avg Power (σ^2) in (1Hz) BW around f_1



repeat 1 to 4 for each freq (f_2, f_3, \dots) for range of interest

- $S_x(f)$ measured in W/Hz or V^2/Hz

- Voltage noise density: $V_n(f) = \sqrt{S_x(f)} \rightarrow V/\sqrt{Hz}$

- Power at freq (e.g., f_2) exactly can not be measured (we take 1Hz BW)


⑤ White noise and noise shaping.

- white noise: noise PSD has the same value at all freq.

- The noise spectrum is shaped by the system transfer func.

- Avg Power (output noise Power) (σ^2) is the area under the output PSD Curve
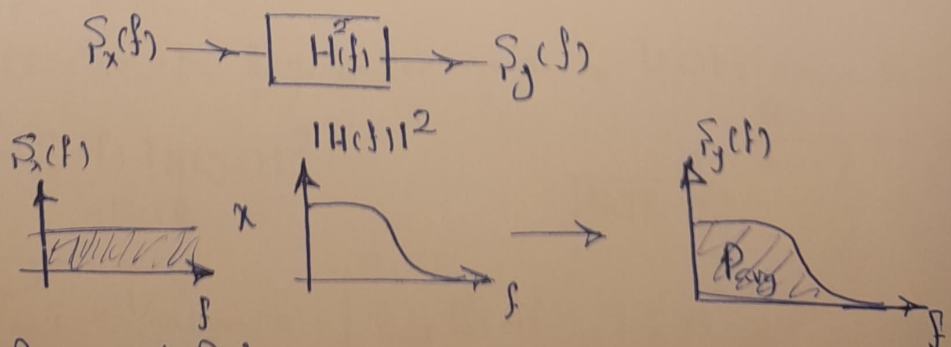
$$P_{avg} = \int_{-\infty}^{\infty} S_y(f) df$$



is wide BW good BW

- Wide BW means more noise Power is integrated

- Wide BW is not good BW \rightarrow amp BW should just fit the sig

⑥ Types of noise.

Page ③


External Noise	Internal Noise		
<ul style="list-style-type: none"> A.k.a. interference noise or man-made noise Unwanted interaction between the outside world Ex. EM interference noise and power supply noise Can be eliminated by careful design, layout, shielding, etc. 	<ul style="list-style-type: none"> Inherent noise due to the fundamental physical properties of the circuit components. <ul style="list-style-type: none"> Can be reduced but cannot be eliminated. 		
	Thermal noise	Shot noise	Flicker noise
	<ul style="list-style-type: none"> Due to thermal excitation of charge carriers White spectral density Independent of DC current Occurs in all resistive elements (including semiconductors) 	<ul style="list-style-type: none"> Due to non-smooth DC current (flow of individual carriers) White spectral density Occurs in pn-junctions (and consequently BJT) 	<ul style="list-style-type: none"> Due to traps in semiconductors affecting DC current flow Significant noise source in MOSFET

⑦ Resistor thermal noise

- From thermodynamics, it can be shown that the spectral density of a resistor thermal noise is

$$V_n^2(f) = S_V(f) = 4kTR$$

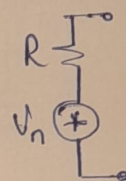$\approx 1.38 \times 10^{-23} \text{ J/K}$




- For $R = 1 \text{ k}\Omega \rightarrow V_n(f) \approx 4 \frac{nV}{\sqrt{\text{Hz}}} \text{ @ } T = 300^\circ \text{K} = 27^\circ \text{C}$

$V_n(f) \approx \sqrt{\frac{R}{1 \text{ k}} \times 4 \frac{nV}{\sqrt{\text{Hz}}}}$

- the norton equivalent $I_n^2(f) = \frac{4kT}{R}$

- For $R = 1 \text{ k}\Omega \rightarrow I_n(f) = 4 \frac{\text{pA}}{\sqrt{\text{Hz}}}$

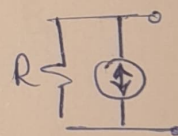
$I_n(f) \approx \sqrt{\frac{1 \text{ k}}{R}} \cdot 4 \frac{\text{pA}}{\sqrt{\text{Hz}}}$



⑧ Noise in RC Circuits.

- in RC Circuits R generates noise $\hat{=}$ Limits noise BW

$$S_{f_{\text{out}}}(f) = \underbrace{S_V(f)}_{\approx 4kTR} |H(j\omega)|^2$$

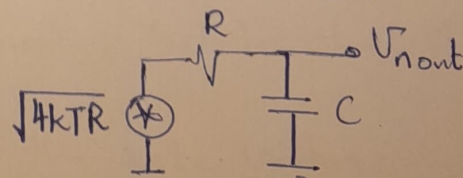

$$\lim_{\omega \rightarrow 0} V_{\text{out}}^2 = V_{\text{out,rms}}^2 = \int_{-\infty}^{\infty} S_{f_{\text{out}}}(f) df = \left[\frac{kT}{C} \right] \# \neq f(R) \text{ why?}$$

when $R \uparrow$, $4kTR \uparrow$, $\text{BW} \downarrow$, noise shaped $S_f = \text{const}$


$\hookrightarrow \text{of } (H)$

- For 1pF Capacitance $\rightarrow V_{rms} = 64 \mu V_{rms}$

$$\# V_{rms} = \sqrt{\frac{1p}{C}} * 64 \mu V_{rms} = 8$$

- for specific BW application (BP)

$\#$ noise limited by R



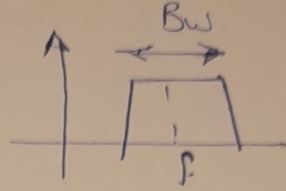


⑨ Equivalent noise BW

- Define an equivalent noise BW (B_N) such that the area under a brick wall response is the same area under the actual spectral density curve

$$V_{rms}^2 = \int_{-\infty}^{\infty} S_n(f) df = 4kTR * B_N = \frac{kT}{C}$$
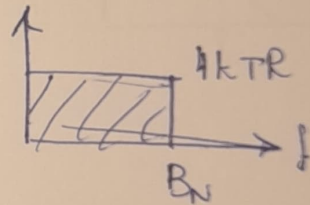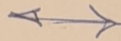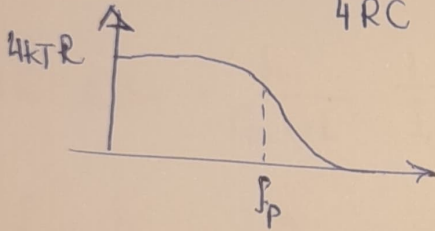
$$\therefore B_N = \frac{1}{4RC} = \frac{\pi}{2} \int_p$$



⑩ MOSFET thermal noise


- MOS has thermal noise due to the resistive nature of the channel

- it can be shown that the noise current spectral density is given by $I_n^2(f) = 4kT \gamma g_m$

\rightarrow similar to a resistor with $R = \frac{1}{\gamma g_m}$

$\rightarrow \gamma$: Mosfet thermal noise Coefficient

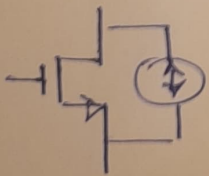$\gamma \approx \frac{2}{3}$ for long channel, $\gamma \approx 1$ for short channel



- the noise current can be referred to the gate voltage

- the relation between I_n and V_n is g_m (not G_m)

$$V_n^2(f) = \frac{4kT\gamma}{g_m} \rightarrow \text{Valid at zero gate current (Low / medium) freq}$$


⑪ flicker noise

- mainly due to dangling bonds at the oxide/silicon interface
- it can be shown that the noise voltage spectral density is given by.

$$V_n^2(f) = \frac{K}{C_{ox}WL} \cdot \frac{1}{f}$$

↗ flicker noise coefficient
↘ scale down herts flicker noise

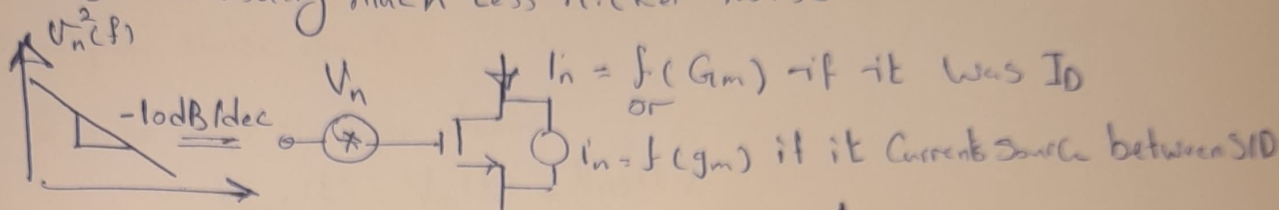
- PMOS has usually much less flicker noise



- flicker noise corner (f_c)

$$4kT \phi g_m = \frac{k}{C_{ox}WL} \cdot \frac{1}{f_c} g_m^2$$
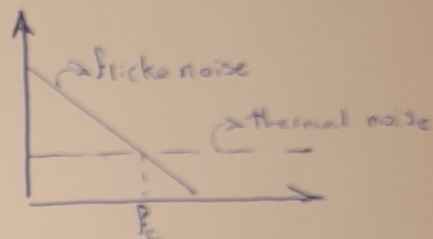
$$f_c = \frac{k}{C_{ox}WL} \cdot g_m \cdot \frac{1}{4kT\phi}$$



- f_c tells which type of noise (thermal/flicker) is dominant for a given signal band

Resistor thermal noise		$V_n(f) = \sqrt{4kTR} = \sqrt{\frac{R}{1k}} \times 4 \frac{nV}{\sqrt{Hz}}$ $I_n(f) = \sqrt{\frac{4kT}{R}} = \sqrt{\frac{1k}{R}} \times 4 \frac{pA}{\sqrt{Hz}}$
MOSFET thermal and flicker noise		$I_n^2(f) = 4kT\phi g_m$ $V_n^2(f) = \frac{K}{C_{ox}WL} \cdot \frac{1}{f}$
RMS noise		$V_{n,out,rms}^2 = 4kTR \times B_N = \frac{kT}{C}$ $B_N = \frac{1}{4RC} = \frac{\pi}{2} f_p$ $V_{n,out,rms} \approx \sqrt{\frac{1p}{C}} \times 64 \mu V_{rms}$

12) Signal to noise ratio.

- is the ratio between Signal Power and noise Power

$$\# \text{ SNR} = \frac{P_{\text{sig}}}{P_{\text{noise}}} = \frac{V_{\text{sig rms}}^2}{V_{\text{n rms}}^2}$$

- SNR is usually expressed in dB

$$\# \text{ SNR} = 10 \log \frac{P_{\text{sig}}}{P_{\text{noise}}} = 20 \log \frac{V_{\text{sig rms}}}{V_{\text{n rms}}}$$

13) multiple noise sources

1. Noise adds in time domain

$$V_{\text{out}}(t) = V_{\text{n1}}(t) + V_{\text{n2}}(t)$$

2. remember: $V_{\text{n}}(t)$ is a random variable

↳ We cannot add rms values

$$V_{\text{out rms}} \neq V_{\text{n1 rms}} + V_{\text{n2 rms}}$$

3. If $V_{\text{n1}}(t)$ and $V_{\text{n2}}(t)$ are uncorrelated (independent) random variables)

$$V_{\text{out rms}}^2 = V_{\text{n1 rms}}^2 + V_{\text{n2 rms}}^2$$

4. The largest noise contributor dominates

$$3^2 + 1^2 \approx 3^2$$



14) output referred noise

- do not compare output noises for compare two designs

- instead compare input referred as output noise depends on design gain

$$\text{or } \frac{V_{\text{out rms}}}{A_v}$$

- Example

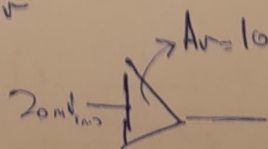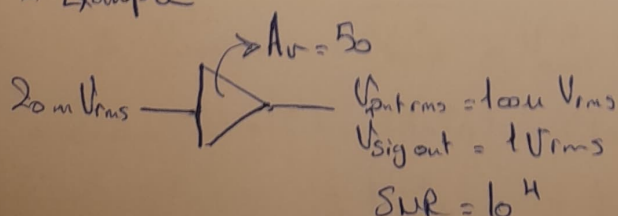

$$\begin{aligned} V_{\text{ntrms}} &= 500 \text{ uVrms} \\ V_{\text{sigout}} &= 200 \text{ mVrms} \\ \text{SNR} &= 4 \times 10^3 \end{aligned}$$

⑮ Noise analysis example (CS with resistive load)

Page ⑦

1 Deactivate the input signal

2 Identify noise sources

↳ Resistor: thermal

↳ Mosfet: Thermal + flicker


3 Find the noise spectral density at output using Superposition

$$① \overline{V_{n_{out}}^2(f)}' = \frac{k}{C_{ox}WL} \cdot \frac{1}{f} \cdot g_m^2 R_D^2$$

$$② \overline{V_{n_{out}}^2(f)}'' = 4kT \gamma g_m [R_D^2 \parallel r_o^2]$$

$$= 4kT \gamma g_m R_D^2$$
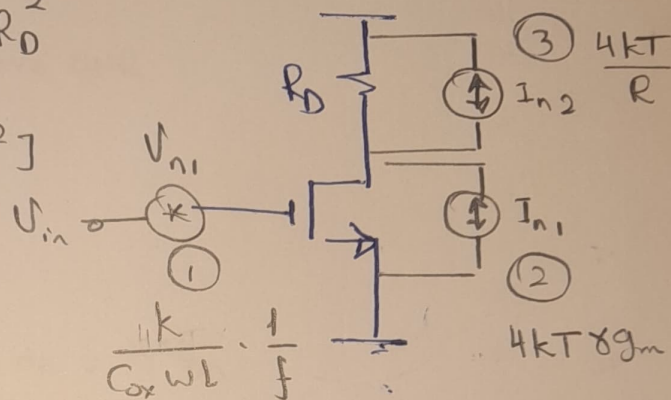
$$③ \overline{V_{n_{out}}^2(f)}''' = \frac{4kT}{R_D} \cdot R_D^2$$



noise densities can not be added unless they all have same shapping (they all depends on the same node = same pole)

$$\therefore \overline{V_{n_{out}}^2(f)} = \left[4kT \gamma g_m + \frac{k}{C_{ox}WL} \cdot \frac{1}{f} \cdot g_m^2 + \frac{4kT}{R_D} \right] R_D^2$$

→ for a fair comparison

$$\overline{V_{n_{in}}^2(f)} = \frac{\overline{V_{n_{out}}^2(f)}}{A_v^2} = \frac{4kT \gamma}{g_m} + \frac{k}{C_{ox}WL} \cdot \frac{1}{f} + \frac{4kT}{g_m^2 R_D}$$

→ assume thermal noise is dominant

$$\overline{V_{n_{out}}^2(f)} \approx 4kT \gamma g_m \left(1 + \frac{1}{g_m R_D} \right) R_D^2$$

→ assume BW is limited by C_L

$$\therefore \overline{V_{n_{out}}^2_{rms}} = \overline{V_{n_{out}}^2} = \overline{V_{n_{out}}^2(f)} \cdot \frac{1}{4R_D C_L} \approx kT (1 + \gamma g_m R_D) \frac{1}{C_L}$$

assume $Q = (1 + \gamma g_m R_D) = (1 + \gamma |A_v|)$

$$\therefore \overline{V_{n_{out}}^2_{rms}} \approx \frac{kTQ}{C_L}$$

- Assume input signal is sinusoidal with amplitude V_p

$$\text{SNR} = \frac{V_{\text{out rms}}^2}{V_{\text{noise rms}}^2} \approx \left(\frac{V_p}{\sqrt{2}} \cdot g_m R_D \right)^2 \cdot \frac{C_L}{kT\Delta} \\ = \frac{V_p^2}{2} \cdot \frac{g_m^2 R_D^2 C_L}{kT\Delta} = \frac{2V_p^2 V_{R_D}^2 C_L}{V^{*2} kT\Delta}$$

- assume $V_{R_D} = \frac{V_{DD}}{2}$

$$\text{SNR} \approx \frac{\cancel{V_p^2} \cancel{V_{DD}^2} C_L}{2V^{*2} kT\Delta} \quad \text{with arrows pointing to } V_p^2 \text{ and } V_{DD}^2 \text{ saying } V_{DD} \text{ improve SNR}$$

- Assume rms output max amplitude $= K V_{DD}$

$$\therefore \text{SNR} = \frac{(K V_{DD})^2 C_L}{kT\Delta} = \frac{(K \cancel{V_{DD}})^2 C_L}{kT(1 + \gamma|A_v|)}$$

- Assume speed spec is fixed (Noise Vs Power)

$$\text{SNR} \approx \frac{V_p^2 V_{DD}^2 C_L}{2V^{*2} kT\Delta}$$

$$\text{GBW} = \frac{g_m}{C_L}$$

↳ To improve SNR by 6 dB (equivalent 1B) in a system limited by thermal noise

$$\therefore C_L \times 4$$

$$\therefore g_m \times 4$$

$$\therefore P_{\text{cons}} \times 4 \rightarrow \text{assuming } V^* \text{ is constant}$$

- Assume P_{cons} is fixed

↳ To improve by 6 dB

$$\therefore C_L \times 4$$

$$\therefore \text{GBW} \times \frac{1}{4} \rightarrow \text{decreasing } V^* \text{ may help But } f_T \downarrow, \text{ Lower Speed}$$