

Spec.			
5T - OTA			
Supply Voltage	1.2 V	Power Consumption	$\leq 30 \mu\text{W}$
Open loop DC voltage gain	$\geq 32 \text{ dB}$	Reference current	10 $\mu\text{A}$
CMRR @ DC	$\geq 70 \text{ dB}$	CM input range low	$\leq 0.6 \text{ V}$
BW	$\geq 200 \text{ kHz}$	CM input range high	$\geq 1 \text{ V}$
Phase Margin	$\geq 70^\circ$	Load	2 pF

- Steps

#### Sizing of M1,2

- 01 | As CMIR is closer to the  $V_{DD}$  rail  $\rightarrow$  use NMOS input pair
- 02 |  $P_{\text{cons}} = V_{DD} I_D \leq 30 \mu\text{W} \rightarrow I_{SS} \leq 25 \mu\text{A} \rightarrow I_{SS} = 20 \mu\text{A} \rightarrow I_D = 10 \mu\text{A}$
- 03 |  $GBW = \frac{g_{m1,2}}{2\pi C_L} \geq 40 \times 200\text{k} = 8 \text{ MHz} \rightarrow g_m \geq 100.5 \mu\text{S} \rightarrow g_m = 150 \mu\text{S} \rightarrow \frac{g_m}{I_D} = 15$
- 04 |  $A_v = g_m \times (r_{o1,2} \parallel r_{o3,4}) \geq 40 \rightarrow R_{\text{out}} \geq 266.7 \text{ k}\Omega \rightarrow \text{Assume } r_{o1,2} = r_{o3,4} = r_o \rightarrow r_o \geq 534 \text{ k}\Omega$
- 05 |  $\therefore g_m r_o \geq 80$  and Assume  $V_{DS1,2} = V_{DD}/3 = 400 \text{ mV} \rightarrow L_{1,2} = 1.5 \mu\text{m}$  and  $W_{3,4} = 7.341 \mu\text{m}$



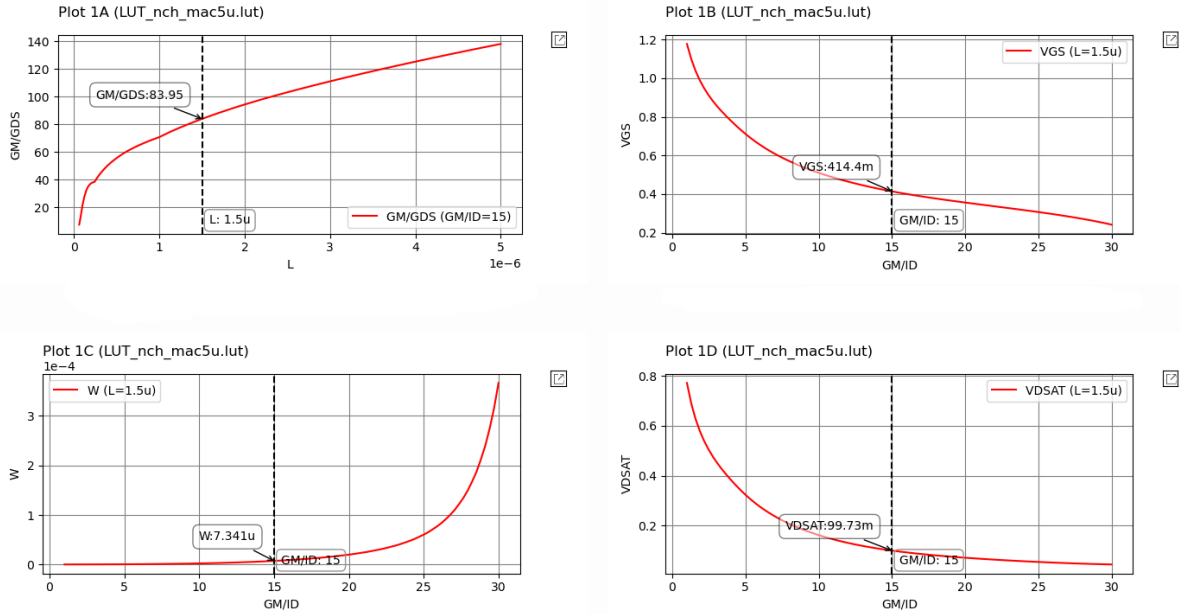
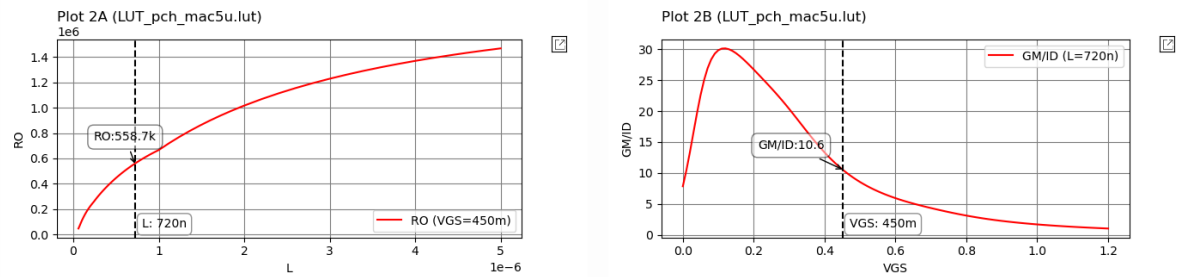


Fig. Sizing of M1,2

#### Sizing of M3,4

- 06 |  $CMIR_H \geq 1 \rightarrow V_{GS1,2} - V_{1,2}^* - V_{SG3,4} + V_{DD} \geq 1 \rightarrow V_{SG3,4} \leq 481 \text{ mV}$
- 07 | If : Choose  $V_{SG3,4} = 450 \text{ mV}$  and  $r_o = 534 \text{ k}\Omega \rightarrow L_{3,4} = 720 \text{ nm}$  and  $W_{3,4} = 4.259 \mu\text{m}$

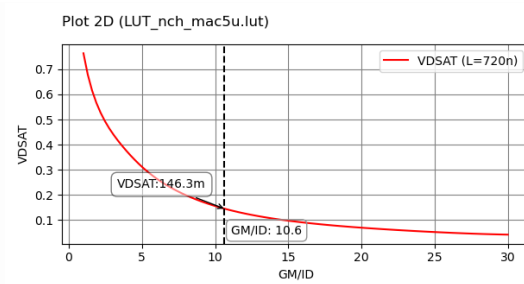

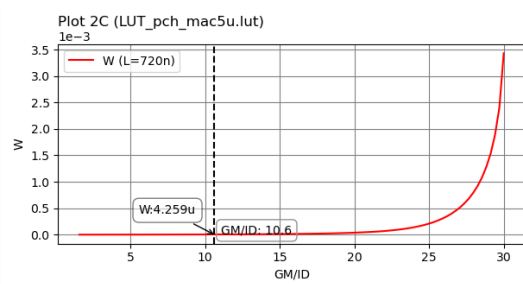



### Sizing of Current Source

08 |  $A_{VCM} = \frac{1}{2g_{m3,4}R_{ss}} = (70 - 32) \text{ dB} = 0.01259 \rightarrow R_{ss} = 380 \text{ k}\Omega$

09 |  $CMIR_L < 0.6 \rightarrow V_{GS1,2} + V_p \leq 0.6 \rightarrow V_p \leq 185 \text{ mV}$

10 |  $R_{ss}$  and  $V_p$  are small  $\rightarrow$  can be achieved using simple Current mirror

11 | Choose  $V_p = V_5^* = 160 \text{ mV} \rightarrow \left(\frac{g_m}{I_D}\right)_3 = 12.5 \rightarrow L_5 = 3 \text{ }\mu\text{m}$  and  $W_5 = 17.27 \text{ }\mu\text{m}$

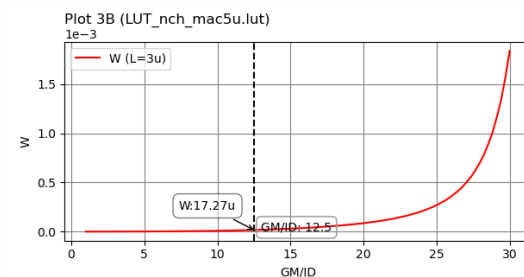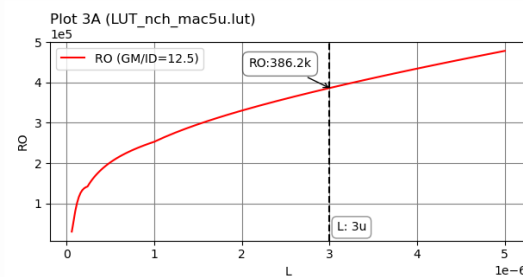



### - Sizing Summary

Sizing Summary			
M	M1,2	M3,4	M5
Rule	Input pair	Active load	Current mirror
L	1.5 $\mu\text{m}$	720 nm	3 $\mu\text{m}$
W	7.341 $\mu\text{m}$	4.259 $\mu\text{m}$	17.27 $\mu\text{m}$
Gmoverid	15	10.6	12.5


### - Results

#### 1. TB and DC Operating Point

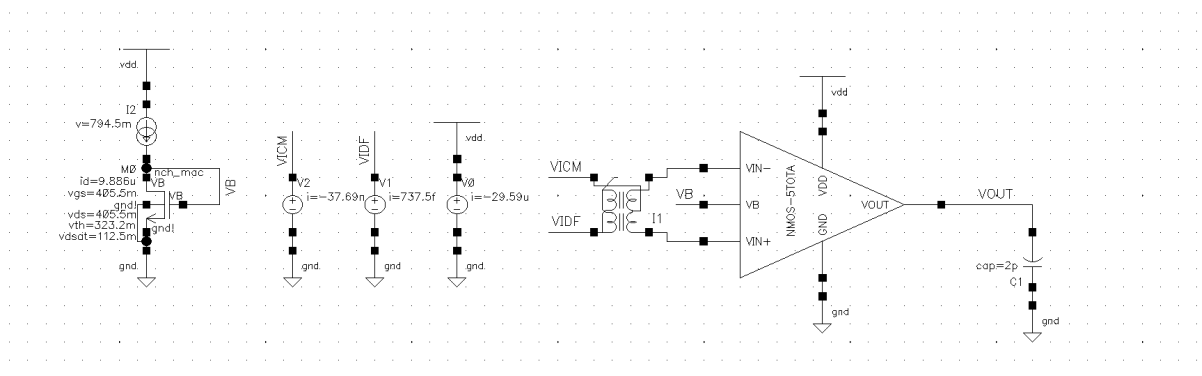

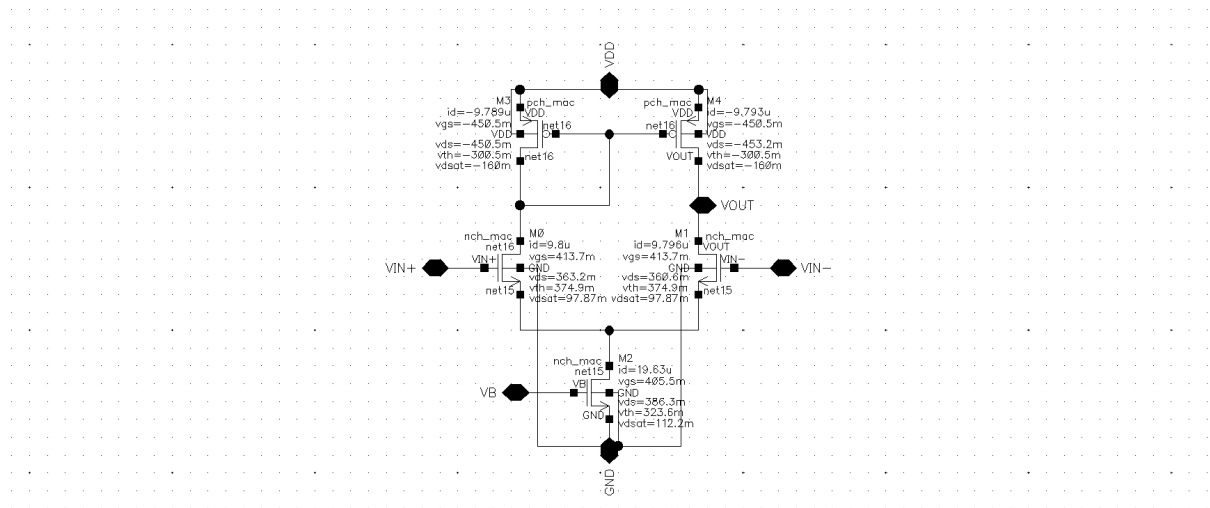


## 2. Differential Small Signal Analysis

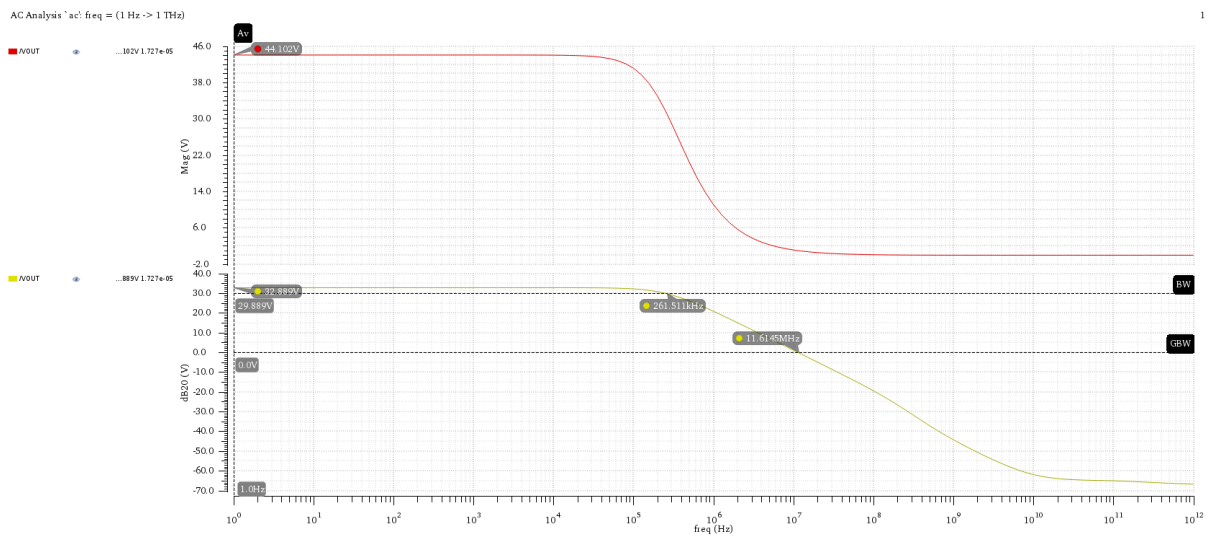


## 3. Common Mode Small Signal Analysis


- AVCM

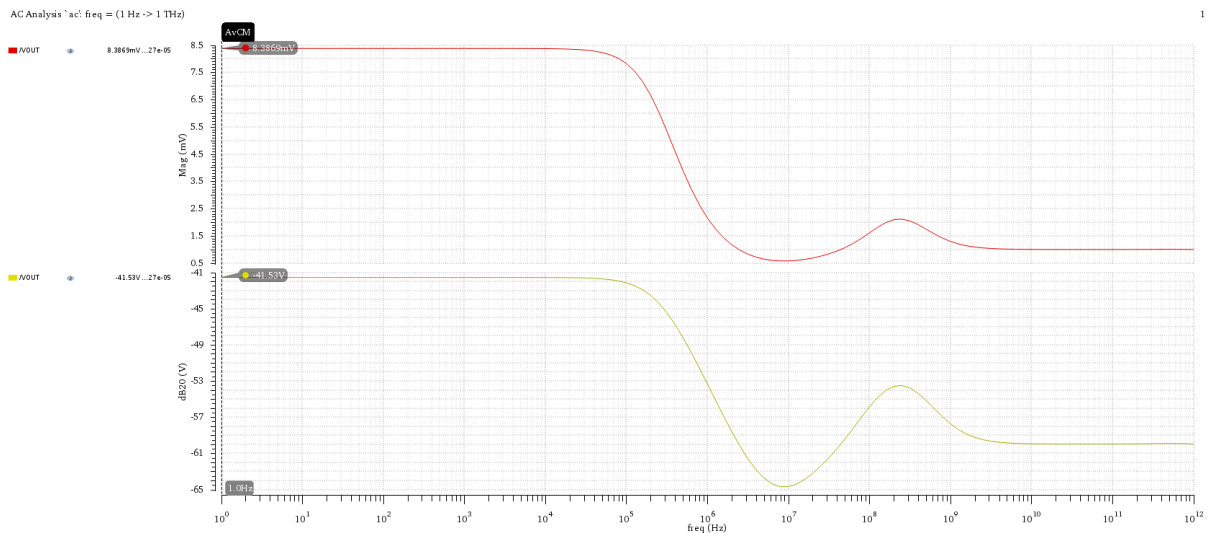

## - CMRR

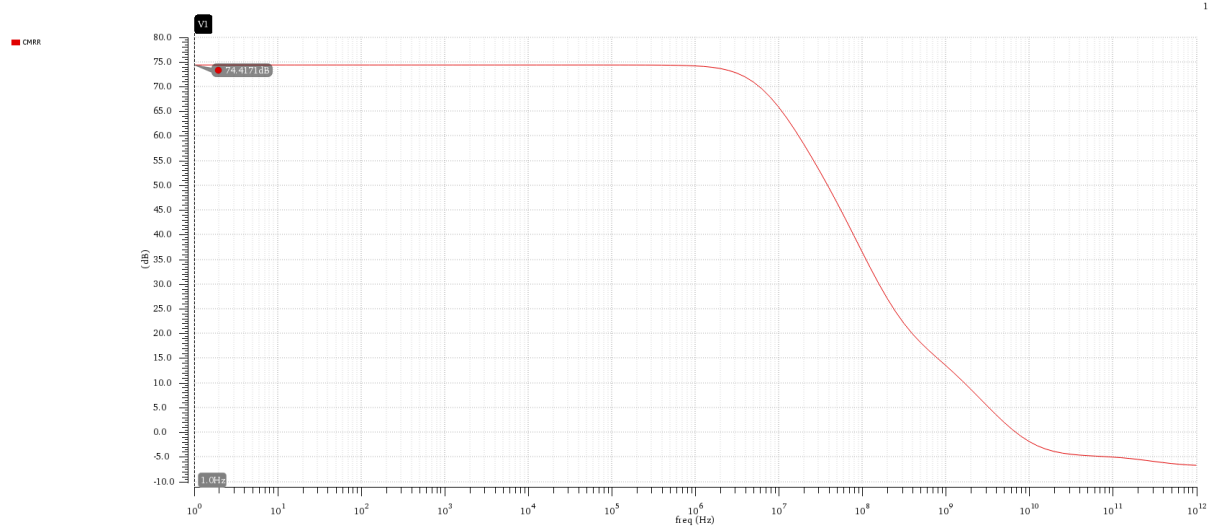

## 4. Differential Large Signal Analysis

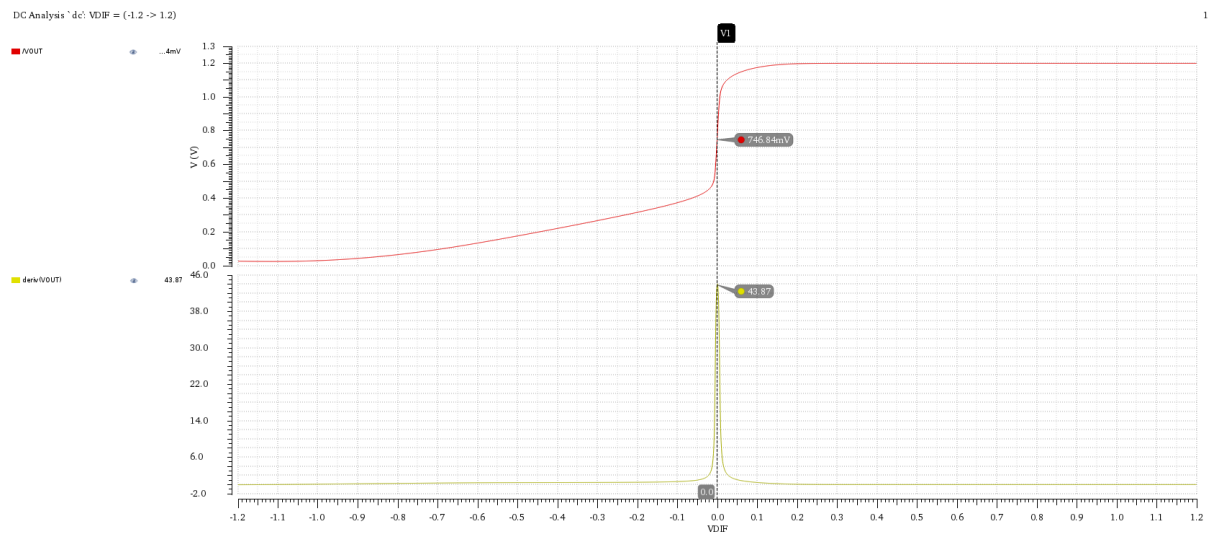

## 5. Common Mode Large Signal Analysis

